

بِسْمِ اللَّهِ الرَّحْمَنِ الرَّحِيمِ

বিস্মিল্লাহির রাহমানির রাহীম



উদ্ভাস

একাডেমিক এন্ড এডমিশন কেয়ার

# Class 12: Physics 2<sup>nd</sup> Paper (Chapter-3)

## Current electricity

Lecture : P-09



# Today's Topics:

- ➔ Kirchhoff's Law
- ➔ Application of Kirchhoff's law
- ➔ Potential Divider
- ➔ Shunt and its application in galvanometer
- ➔ Few symbols of components used in circuit
- ➔ Mathematical Problems
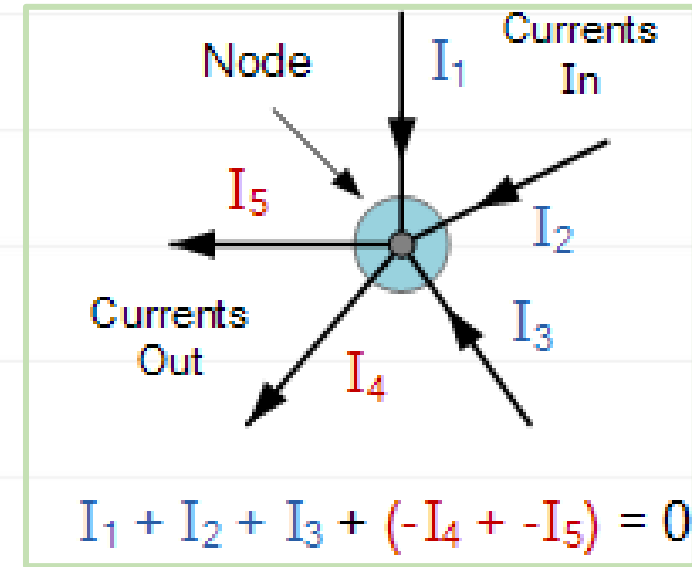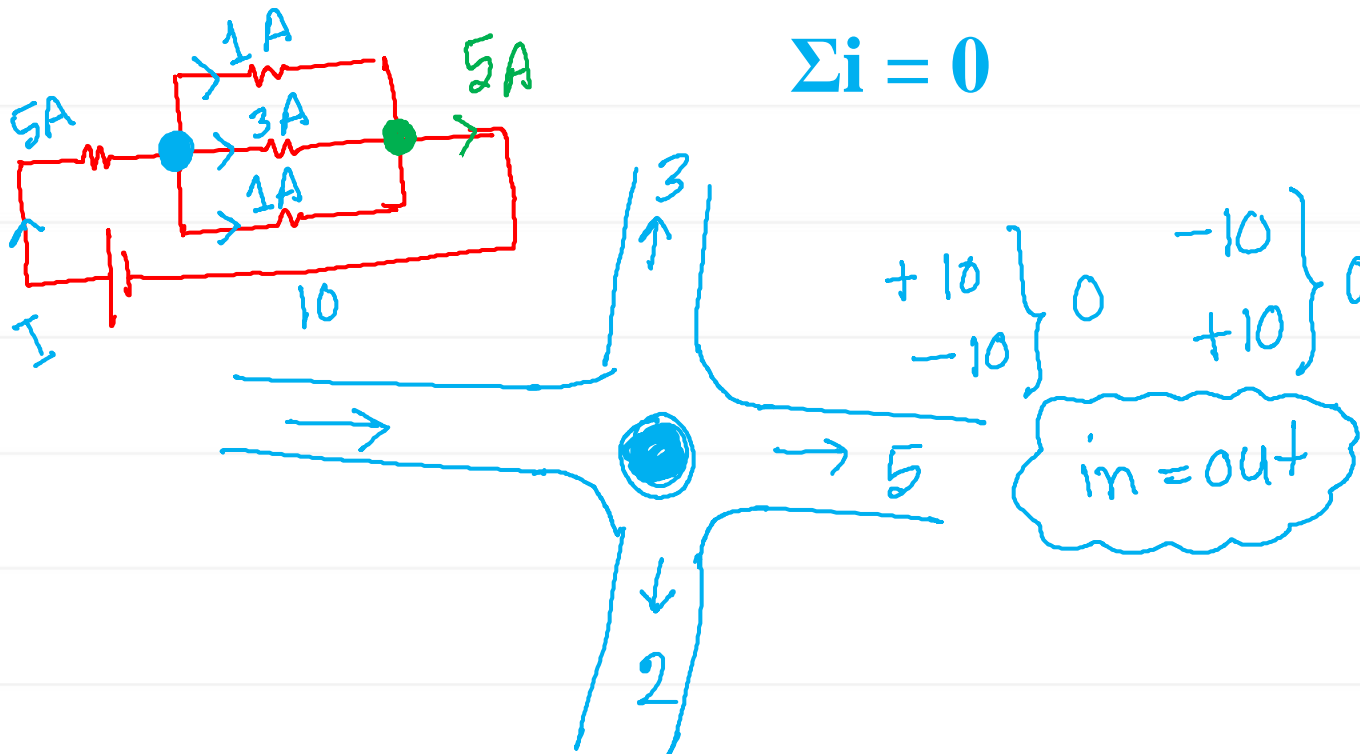
# Kirchhoff's 1<sup>st</sup> law

To solve critical circuits Kirchhoff's laws are us rather than ohm's law.

**1<sup>st</sup> law:** The algebraic sum of currents in a network of conductors meeting at a point is zero.



# Poll Question 01

Which one is Kirchhoff's 1<sup>st</sup> law?

~~(a)  $\Sigma i_1 + i_2 + i_3 + i_4 + \dots = 0$~~

(b)  $\Sigma i_1 + i_2 - i_3 + i_4 + \dots = 0$

(c)  $\Sigma i_1 + i_2 + i_3 - i_4 + \dots = 0$

(d)  $\Sigma i_1 - i_2 + i_3 + i_4 - \dots = 0$

$$\sum_{n=0}^{n=R} n$$

per day

income  $\rightarrow$  5/-

expense  $\rightarrow$  5/-

---

+5 -5


saving = 0

(+5) + (-5)

= 0
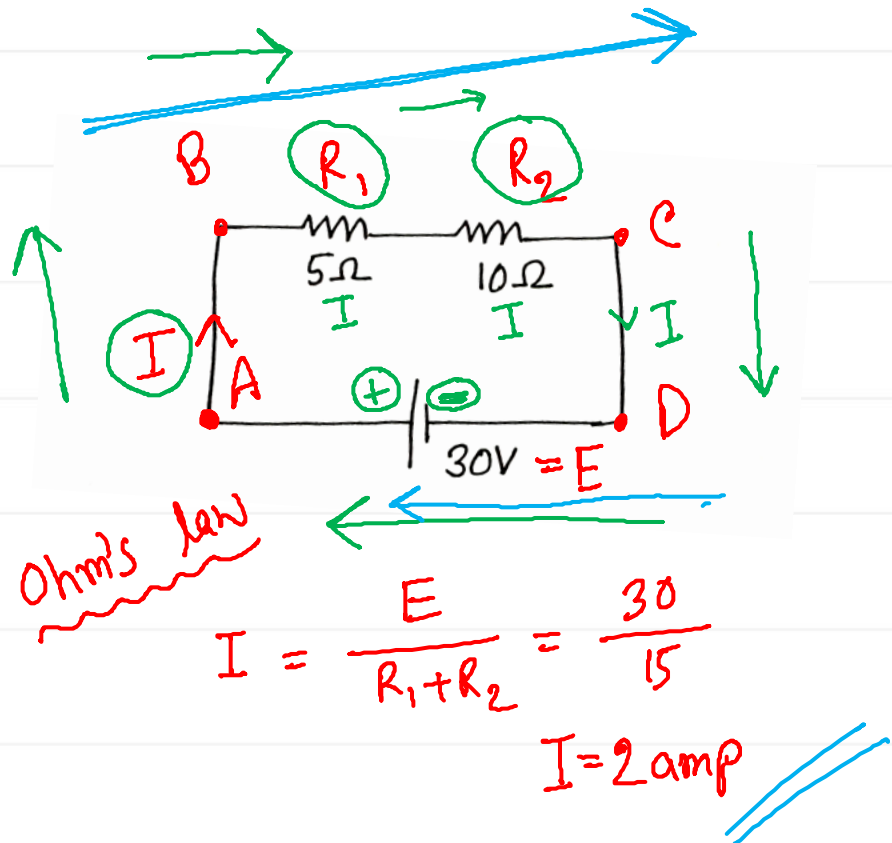
# Kirchhoff's 2<sup>nd</sup> law

**2<sup>nd</sup> law:** The directed sum of the potential differences (voltages) around any closed loop is zero.



$$\Sigma E = \Sigma iR$$


$$\Sigma E - \Sigma iR = 0$$

↻ or ↻  
ABCD loop  
AB → X  
BC →  $IR_1; IR_2$   
CD → X  
DA → -30


↻  
ABCD loop  
$$+5I + 10I - 30 = 0$$
  
$$15I = 30$$
  
$$I = 2 \text{ amp}$$

# Mathematical Example 01 on Kirchhoff's 2<sup>nd</sup> law

Loop-1, Voltage Source-1

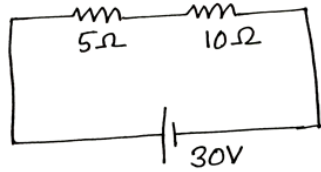

Step-1:

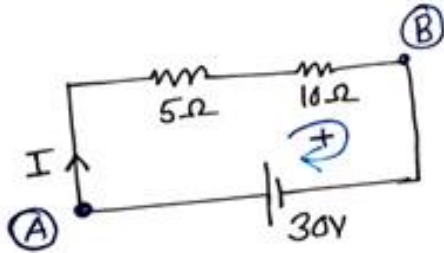

$$5I + 10I - 30 = 0 \Rightarrow 15I = 30$$

$$\therefore I = 2 \text{ amp}$$


A বিন্দু থেকে clockwise ঘুরে A বিন্দুতে থাম।

যদি B থেকে ঘুরতাম-

$$-30V + 5I + 10I = 0 \Rightarrow I = 2 \text{ amp}$$

Step-1: ↻ or ↻

Step-2: Kirchhoff's 2<sup>nd</sup> law

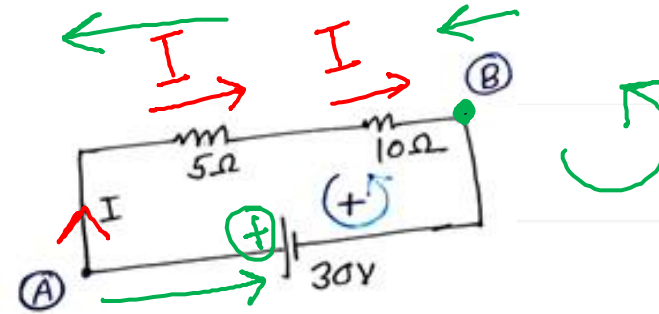

$$-10I - 5I + 30 = 0 \Rightarrow -15I + 30 = 30$$

$$\therefore I = 2 \text{ amp} \checkmark$$

A বিন্দু থেকে clockwise ঘুরে A বিন্দুতে থাম।

যদি A থেকে ঘুরতাম-

$$+30 - 10I - 5I = 0 \Rightarrow I = 2 \text{ amp}$$




# Poll Question 02

How much current will enter or out from the 6<sup>th</sup> branch?


- ~~(a) 3 in~~
- (b) 3 out
- (c) 7 in
- (d) 7 out

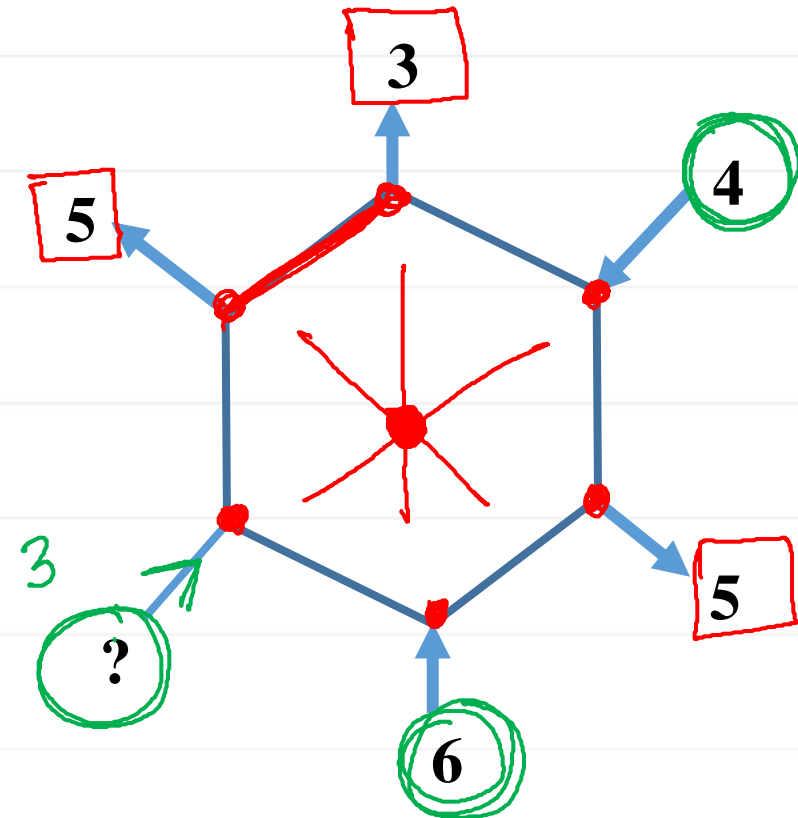input = output  
 $out = 5 + 3 + 5 = 13$   
 $in = 4 + 6 = 10 + 3$


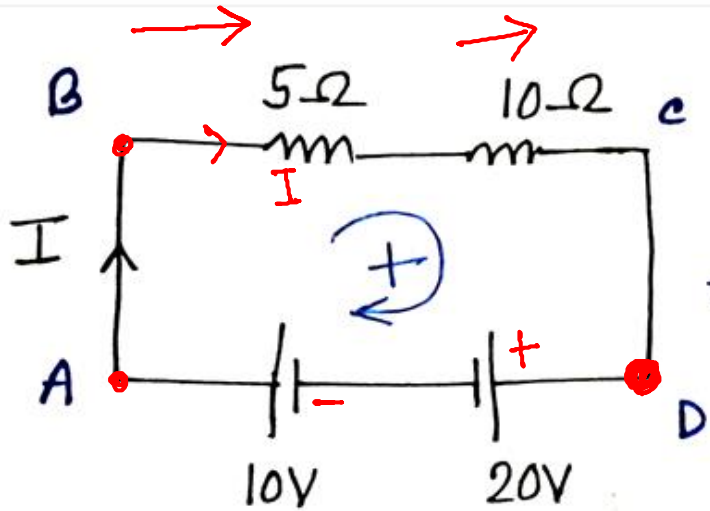
# Math 01

How Much current is passing through each cell?




DABCD (2)

$$+20 - 10 + 5I + 10I = 0$$

$$\Rightarrow 15I = -10$$


$$\therefore I = -10/15 = -2/3 = -0.67 \text{ amp}$$

-ve?


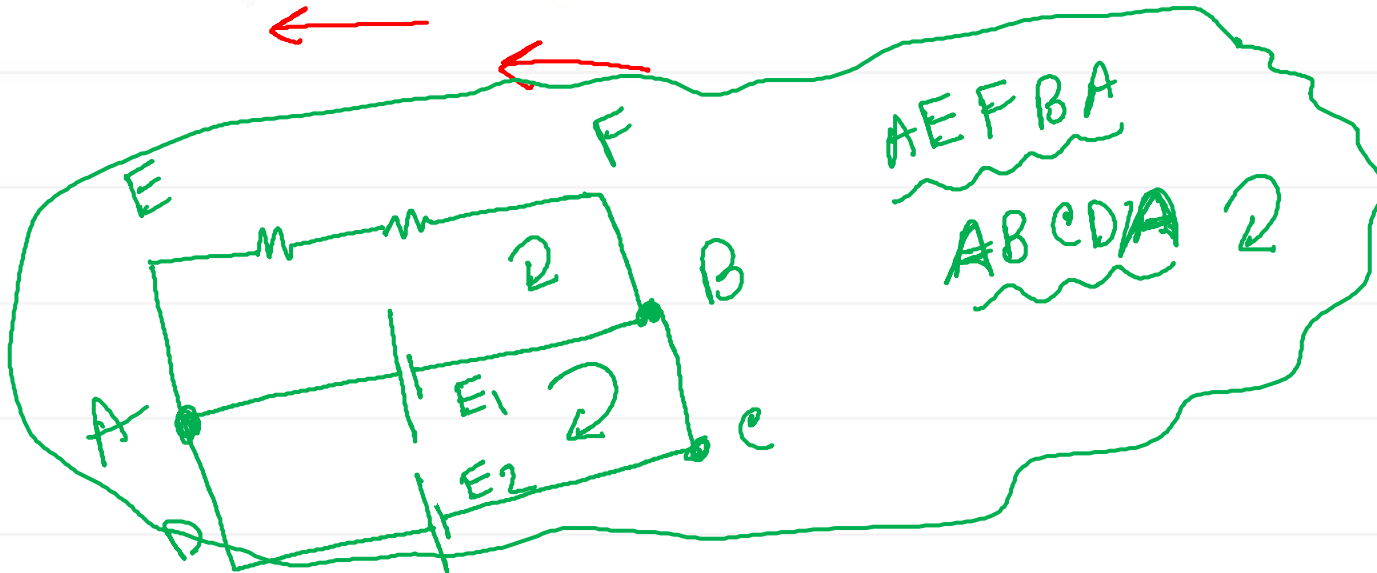


# Mathematical Example 02 on Kirchoff's 2<sup>nd</sup> law

Loop-1, Voltage Source-1++

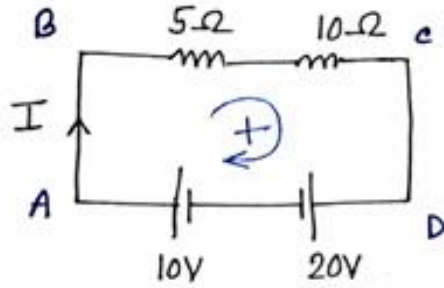

Or,

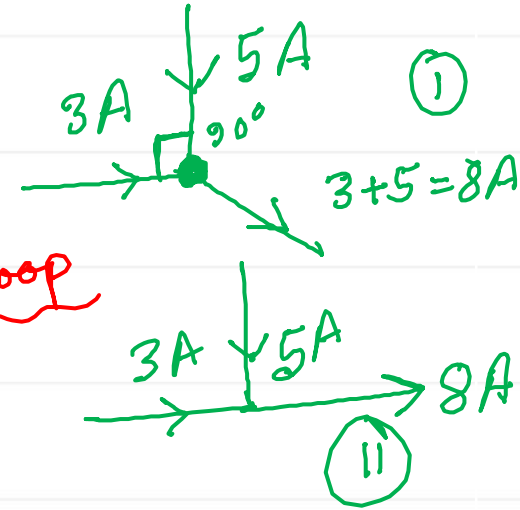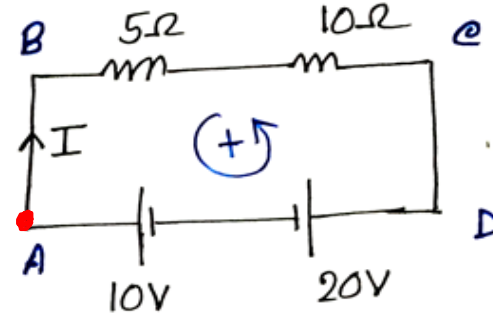

ABCD A লুপ-

$$+5I + 10I + 20 - 10 = 0$$

$$\Rightarrow 15I + 10 = 0$$

$$\Rightarrow I = -\frac{10}{15} = -\frac{2}{3}A$$

$$\therefore I = -0.67A$$

-ve মানে direction যা ধরা হয়েছে, current এর flow উল্টাবাবে হবে।

~~ABCD A~~ লুপ-

ADCBA loop

$$+10 - 20 - 10I - 5I = 0$$

$$\Rightarrow -10 - 15I = 0$$

$$\Rightarrow I = -\frac{10}{15}$$


$$\therefore I = -0.67A$$

-ve value এর meaning direction opposite.

N.B.: Current এর direction both case এ same ধরে নেয়া। Loop যেভাবেই ঘুরুক answer same ই আসবে।
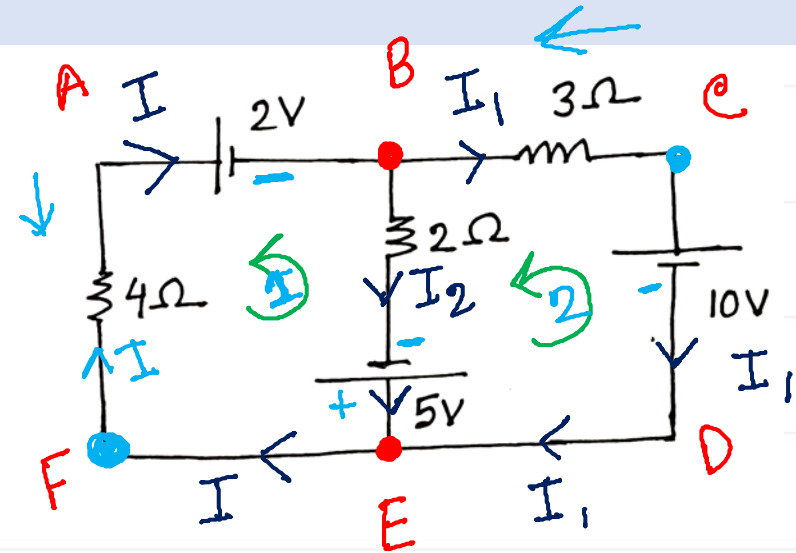
# Math 02

Taking anti clockwise direction find out how much current is passing through each cell?



FEBAF

$$+5 - 2I_2 - 2 - 4I = 0$$

$$\Rightarrow 3 - 2I_2 - 4(I_1 + I_2) = 0$$

$$\Rightarrow 3 - 6I_2 - 4I_1 = 0$$

$$\Rightarrow 4I_1 + 6I_2 = 3 \quad \text{--- (i)}$$

CBEDC

$$-3I_1 + 2I_2 - 5 - 10 = 0$$

$$\Rightarrow 3I_1 - 2I_2 = -15 \quad \text{--- (ii)}$$

B node

$$I = I_1 + I_2 \quad \text{--- 1st}$$


E node

$$I_2 + I_1 = I \quad \text{--- 1st}$$

$$\textcircled{i}, \textcircled{ii} \quad I_1 = -\frac{42}{13} = -3.231 \text{ A}$$

$$I = I_1 + I_2 = -0.578 \text{ A} \quad I_2 = \frac{69}{26} = 2.654 \text{ A}$$
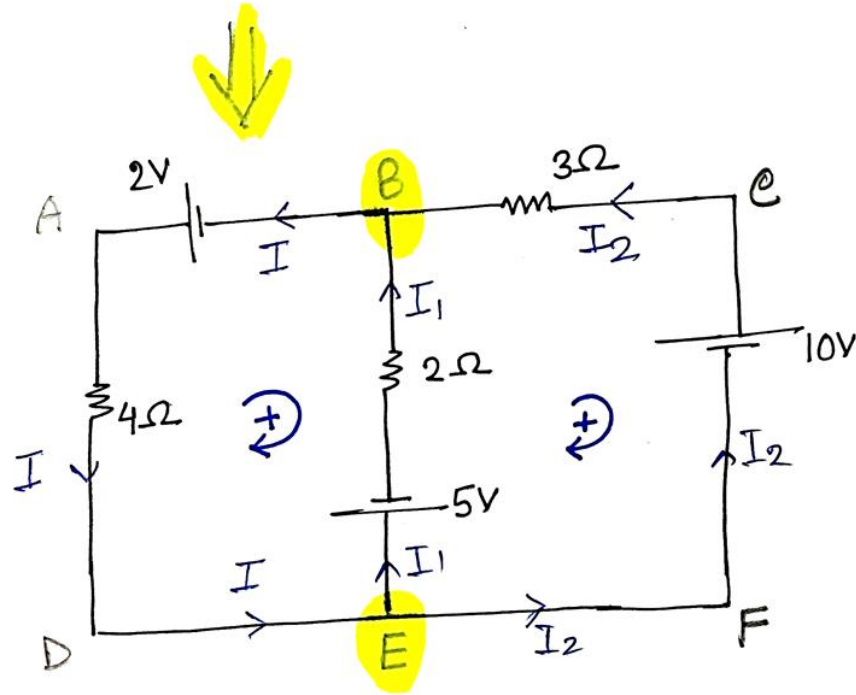
# Mathematical Example 03 on Kirchhoff's 2<sup>nd</sup> law



B এবং E node এ-

$$I = I_1 + I_2 \dots \dots (i) \text{ [কার্শফের 1<sup>st</sup> law]}$$

ছবিতে মোট ৩টি Loop আছে। আমরা আপাতা ২টি নিব।

**ABEDA Loop,**

$$+2 - 2I_1 - 5 - 4I = 0$$

$$\Rightarrow -3 - 2I_1 - 4I_1 - 4I_2 = 0 \dots \dots (i)$$

$$\Rightarrow 6I_1 + 4I_2 = -3 \dots \dots (ii)$$

**BCFEB Loop,**

$$-3I_2 + 10 + 5 + 2I_1 = 0$$

$$\Rightarrow 15 + 2I_1 - 3I_2$$


$$\Rightarrow 2I_1 - 3I_2 = -15 \dots \dots (iii)$$

Solving equation (ii) & (iii),

$$I_1 = -\frac{69}{26} = -2.654 \text{ amp}$$

$$I_2 = \frac{42}{13} = 3.231 \text{ amp}$$
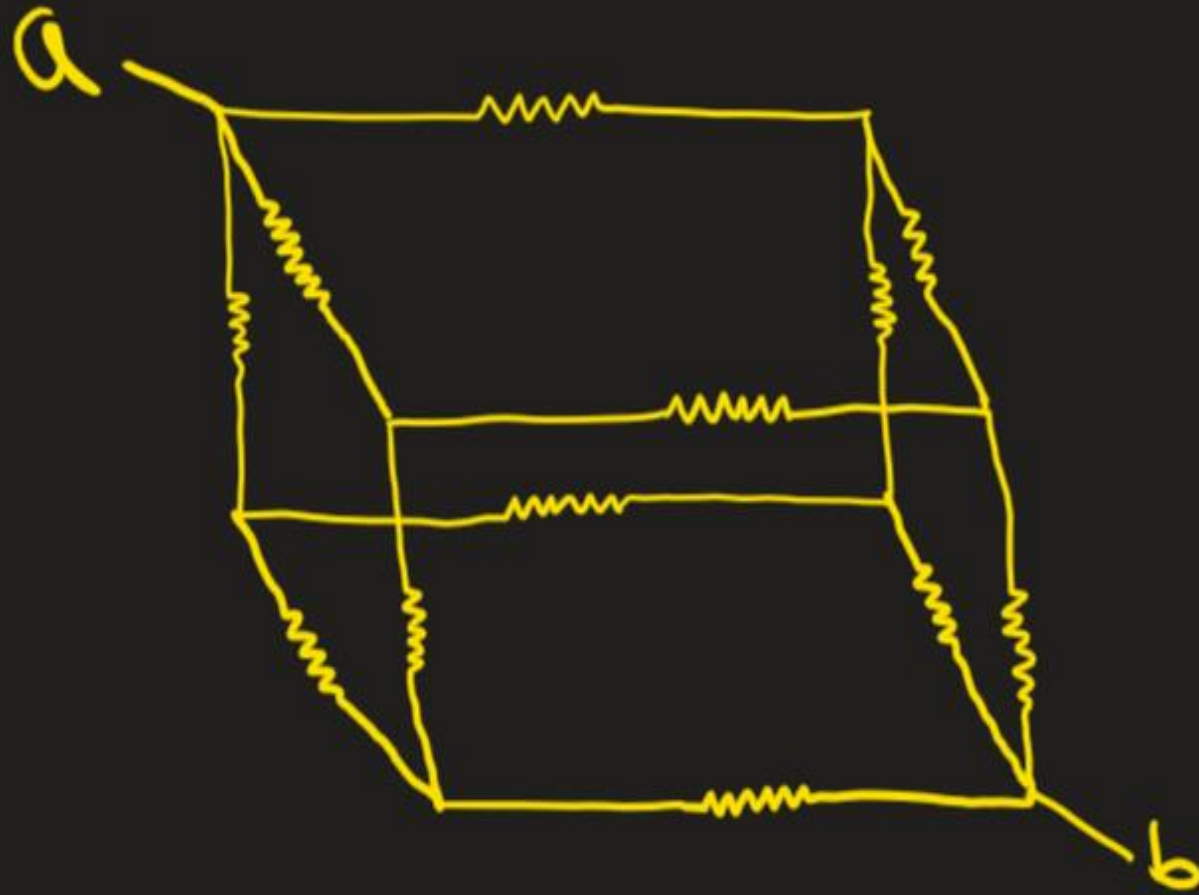
$$\therefore I = \frac{15}{26} = 0.577 \text{ amp}$$





Ques: if all the resistors are of equal value ( $R$ ).

Then,  $R_{ab} = ?$


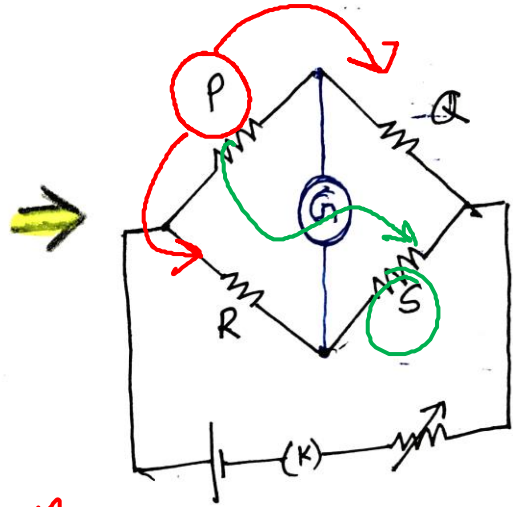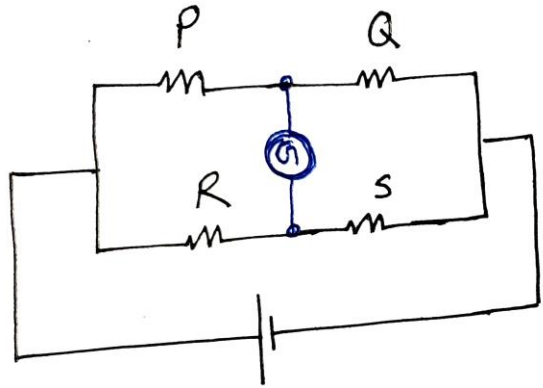
# Use of Kirchhoff's law in Wheatstone bridge



$I_g = 0$  [cond.]  
Equilibrium achieved

$$\frac{P}{Q} = \frac{R}{S}$$

or

$$\frac{P}{R} = \frac{Q}{S}$$


$$\frac{P}{S} = \frac{R}{Q}$$

$$I = I_1 + I_2$$

$$I_1 = I_g + I_3$$

$$I_2 + I_g = I_4$$

$$I_3 + I_4 = I$$

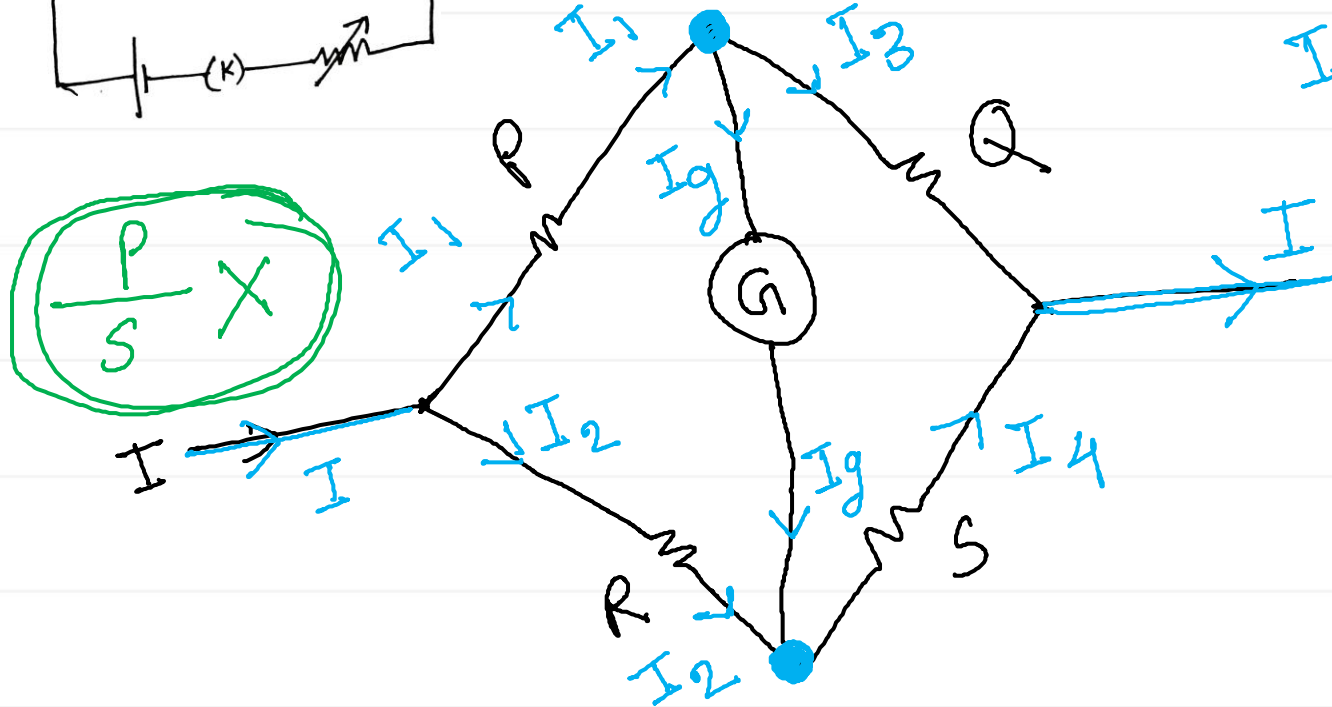



# Poll Question 03

If  $R_1$ ,  $R_2$ ,  $R_3$  are 5, 2, 15 ohms respectively,  
to attain equilibrium how much resistance is to be applied on the 4<sup>th</sup> arm?

$$\frac{P}{Q} = \frac{R}{S} \quad \text{OR} \quad \frac{P}{R} = \frac{Q}{S}$$


(a) 3 ohm


(b) 4 ohm

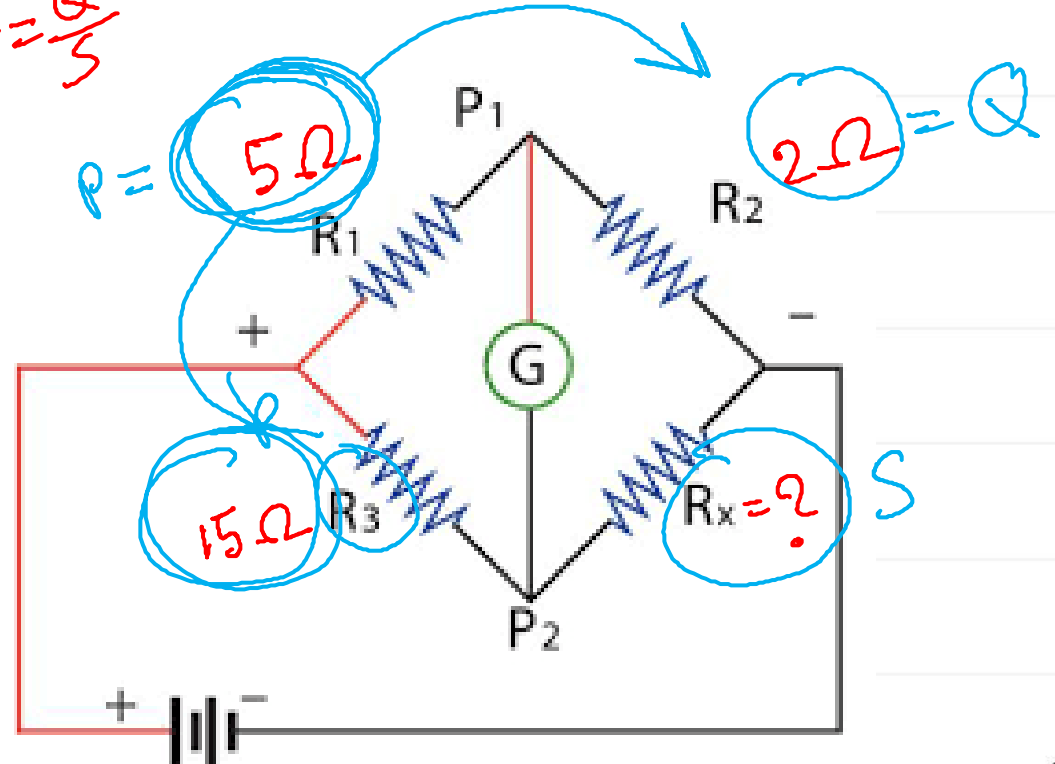(c) 7.5 ohm

~~(d) 6 ohm~~


$$\frac{5}{2} = \frac{15}{S} \quad \times 3 \rightarrow \frac{5}{15} = \frac{2}{S} \quad \times 3 \rightarrow \frac{5}{5} = \frac{2 \times 3}{S} \rightarrow 1 = \frac{6}{S} \rightarrow S = 6$$




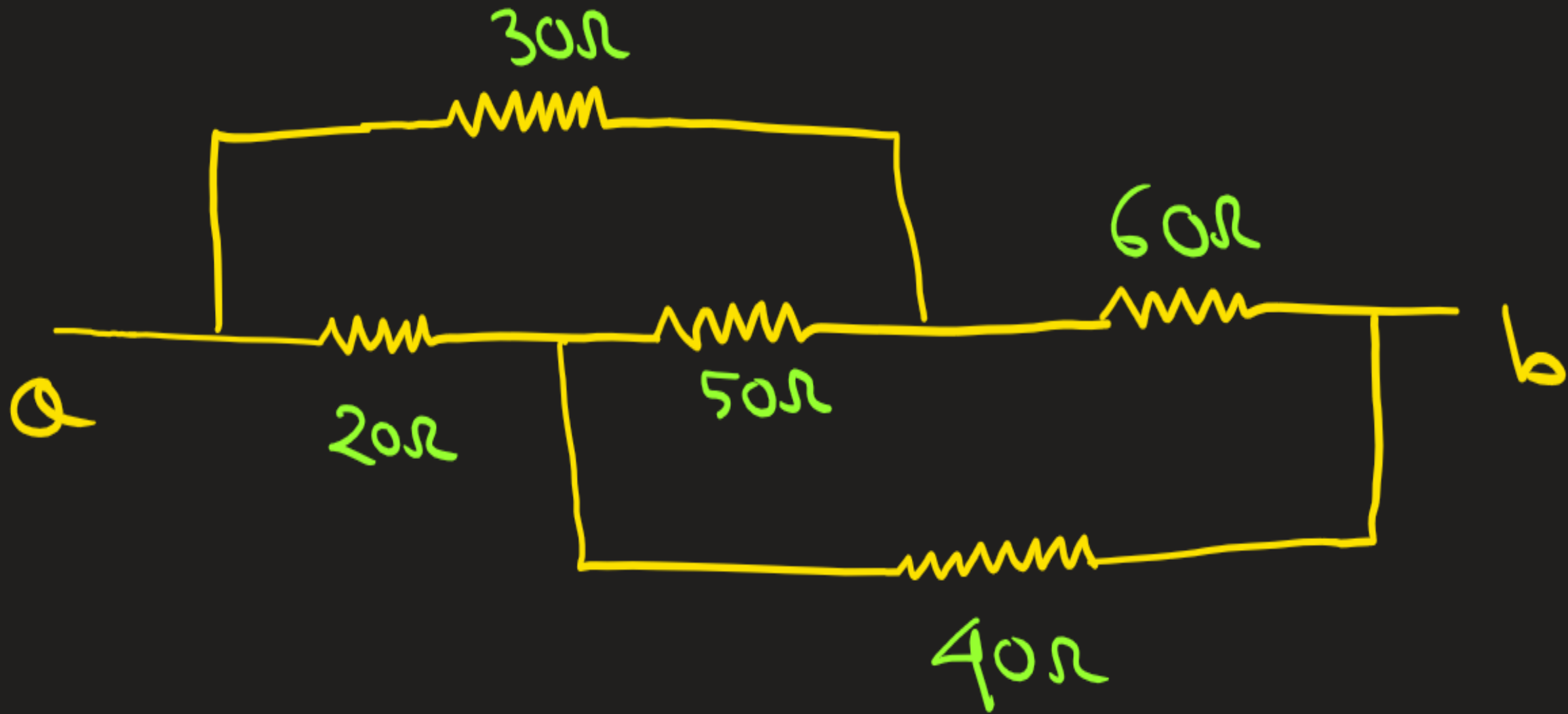


Ques.:  $R_{ab} = ?$


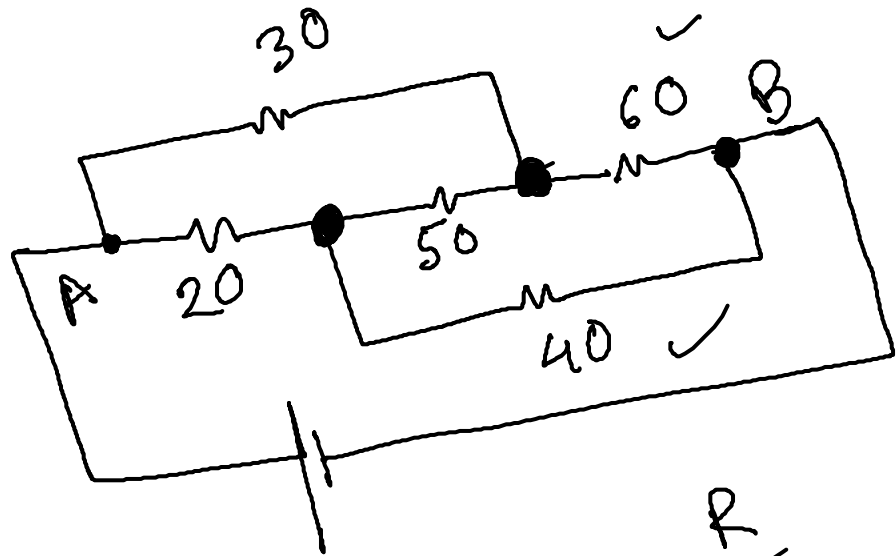
$$R_{ab} = \left( \frac{1}{90} + \frac{1}{60} \right)^{-1}$$



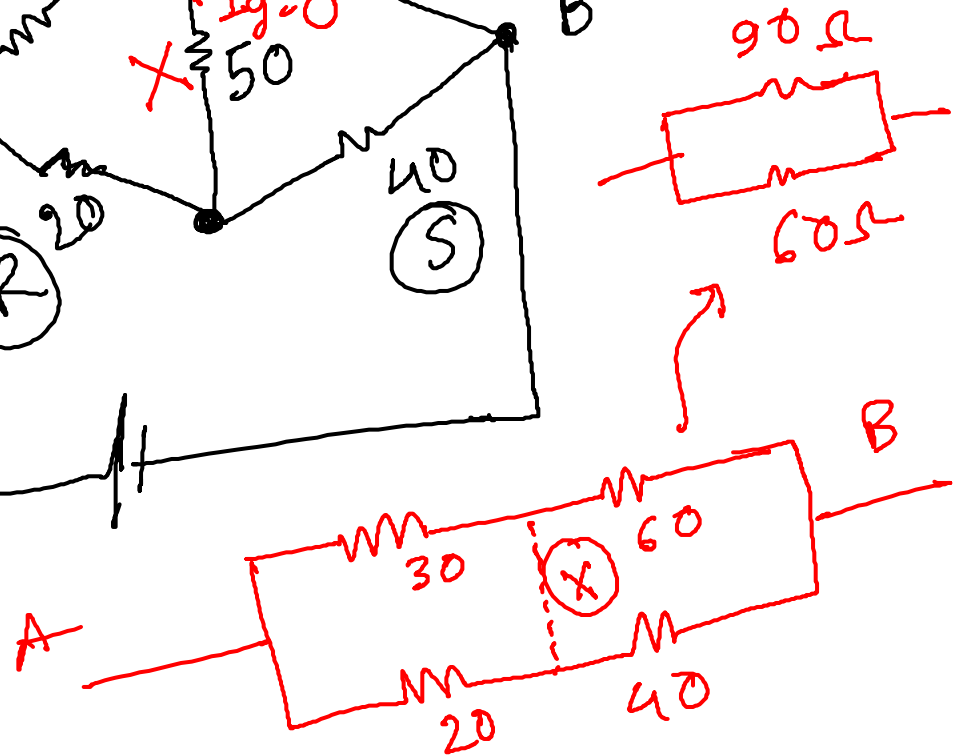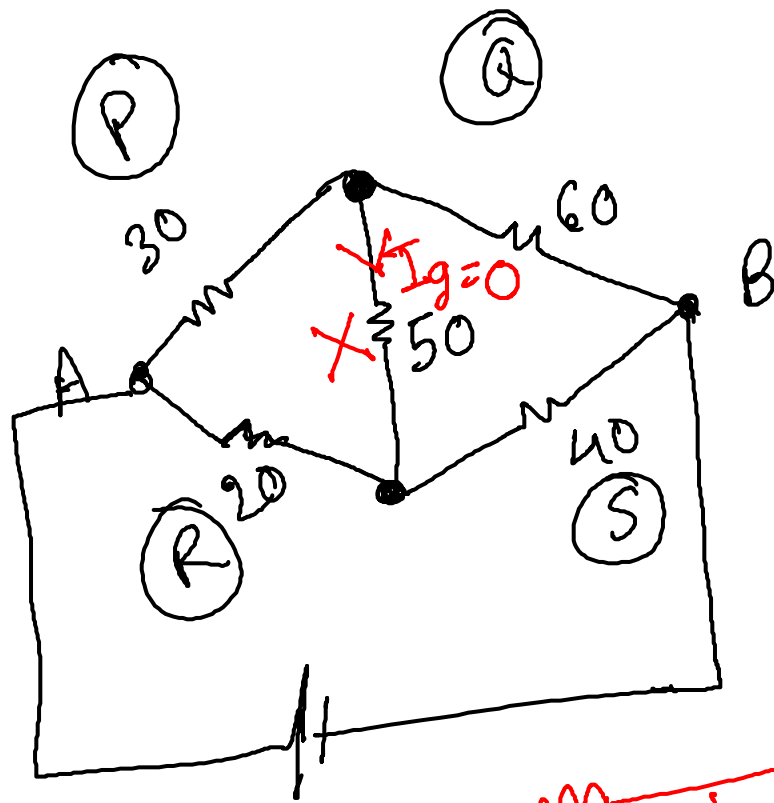$\therefore \frac{P}{Q} = \frac{R}{S}$   
 Equilibrium  
 $I_g = 0$



# Potential Divider

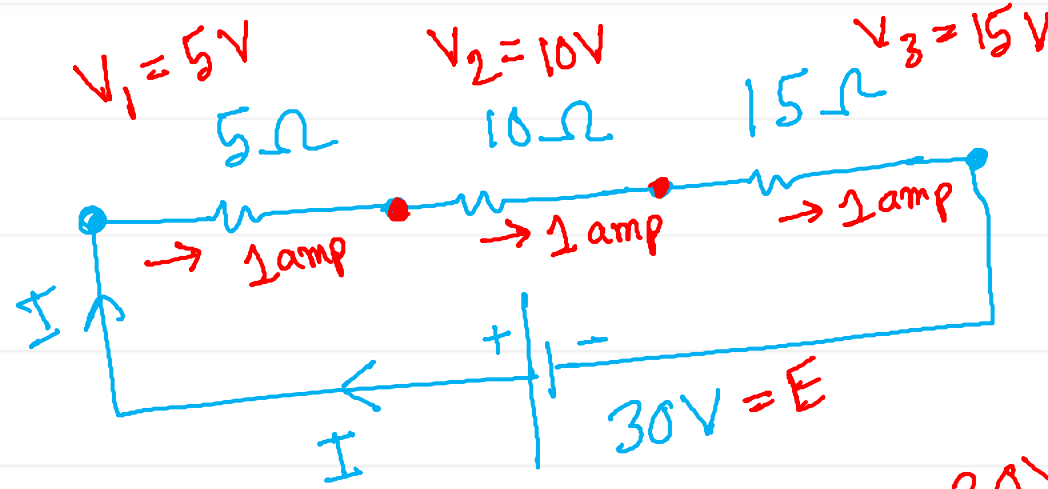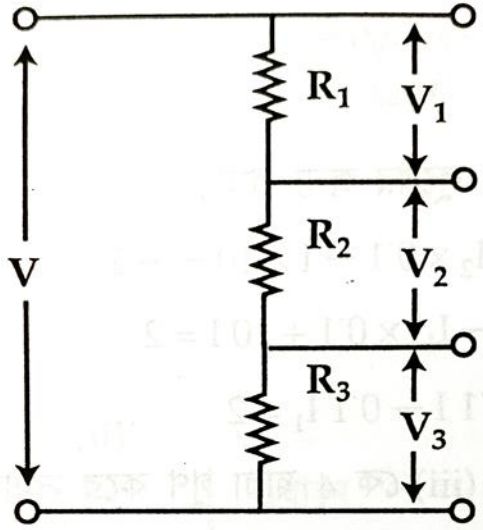


$$I = \frac{30}{30} = 1 \text{ amp}$$

$$V_1 + V_2 + V_3 = 30V$$
$$E = 30V$$
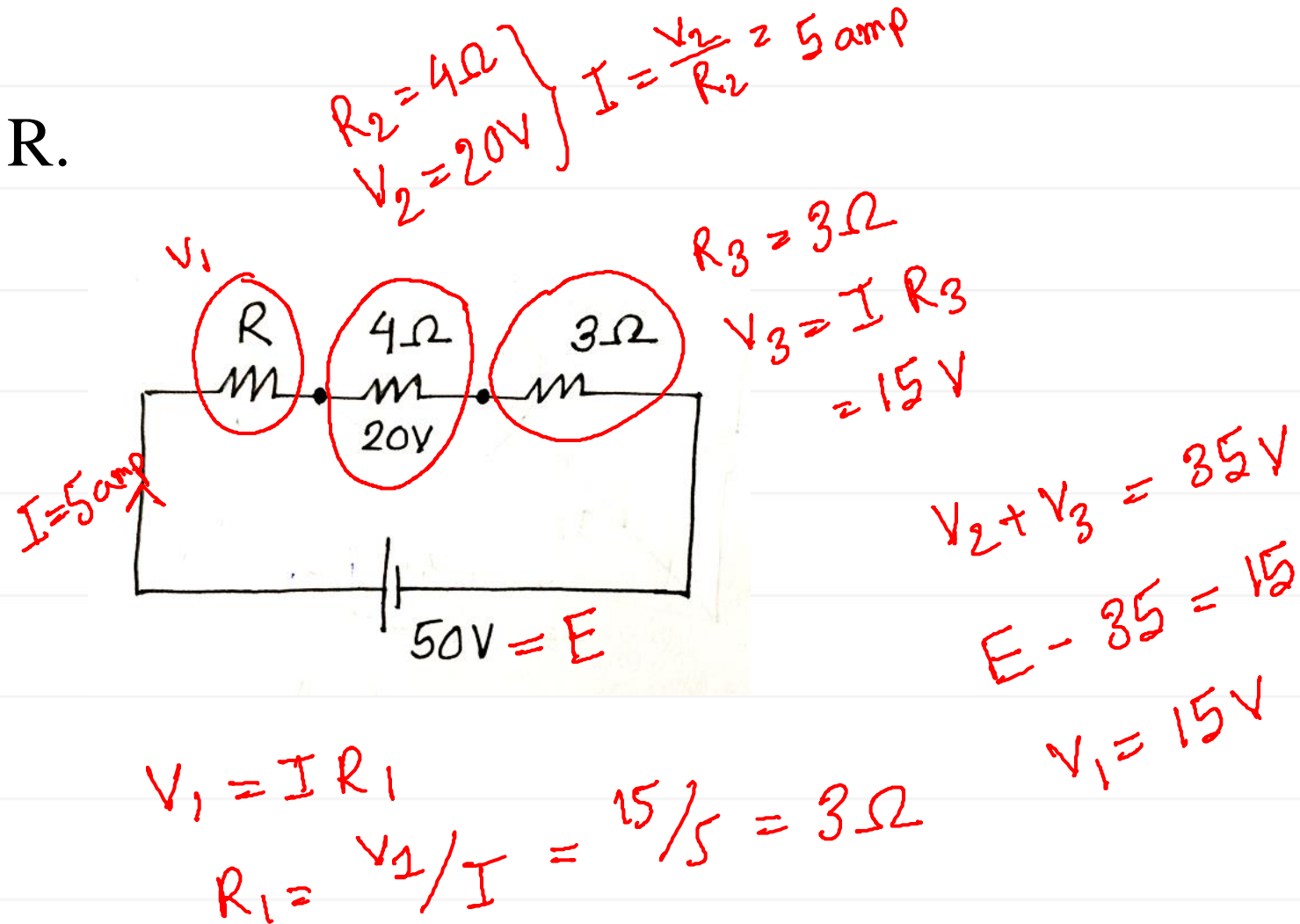
# Poll Question 04



Find out value of R.

- ~~(a) 3 ohm~~
- (b) 4 ohm
- (c) 5 ohm
- (d) 6 ohm


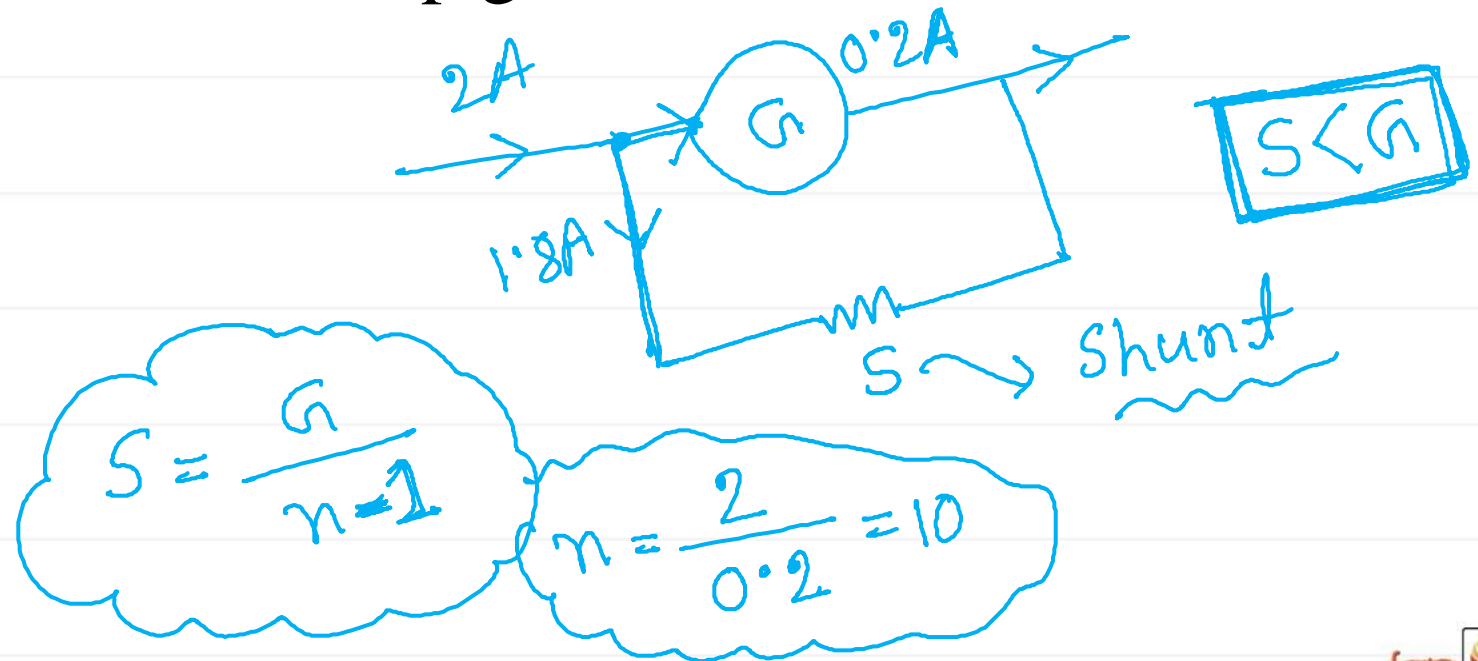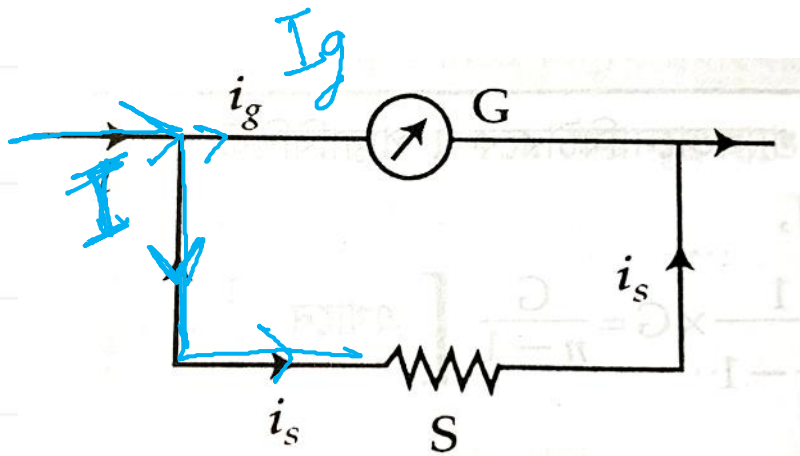
# Shunt

In electronics, a shunt is a device that creates a low-resistance path for electric current, to allow it to pass around another point in the circuit. The resistor of very low but accurately known resistance, is placed in **parallel** with a galvanometer, so that virtually all of the current to be measured will flow through the resistor and keep galvanometer safe.



$$S = \frac{G}{n-1}$$

$$n = \frac{2}{0.2} = 10$$

# Math 03

A galvanometer of 100 ohm resistance can safely measure 10mA current. How we can measure 10 A current with this galvanometer?


$$G = 100 \Omega$$

$$I = 10 \text{ mA} = 10 \times 10^{-3} \text{ A}$$

$$I' = 10 \text{ A}$$

$$n = \frac{I'}{I} = \frac{10}{10 \times 10^{-3}} = 10^3$$


$$S = ?$$

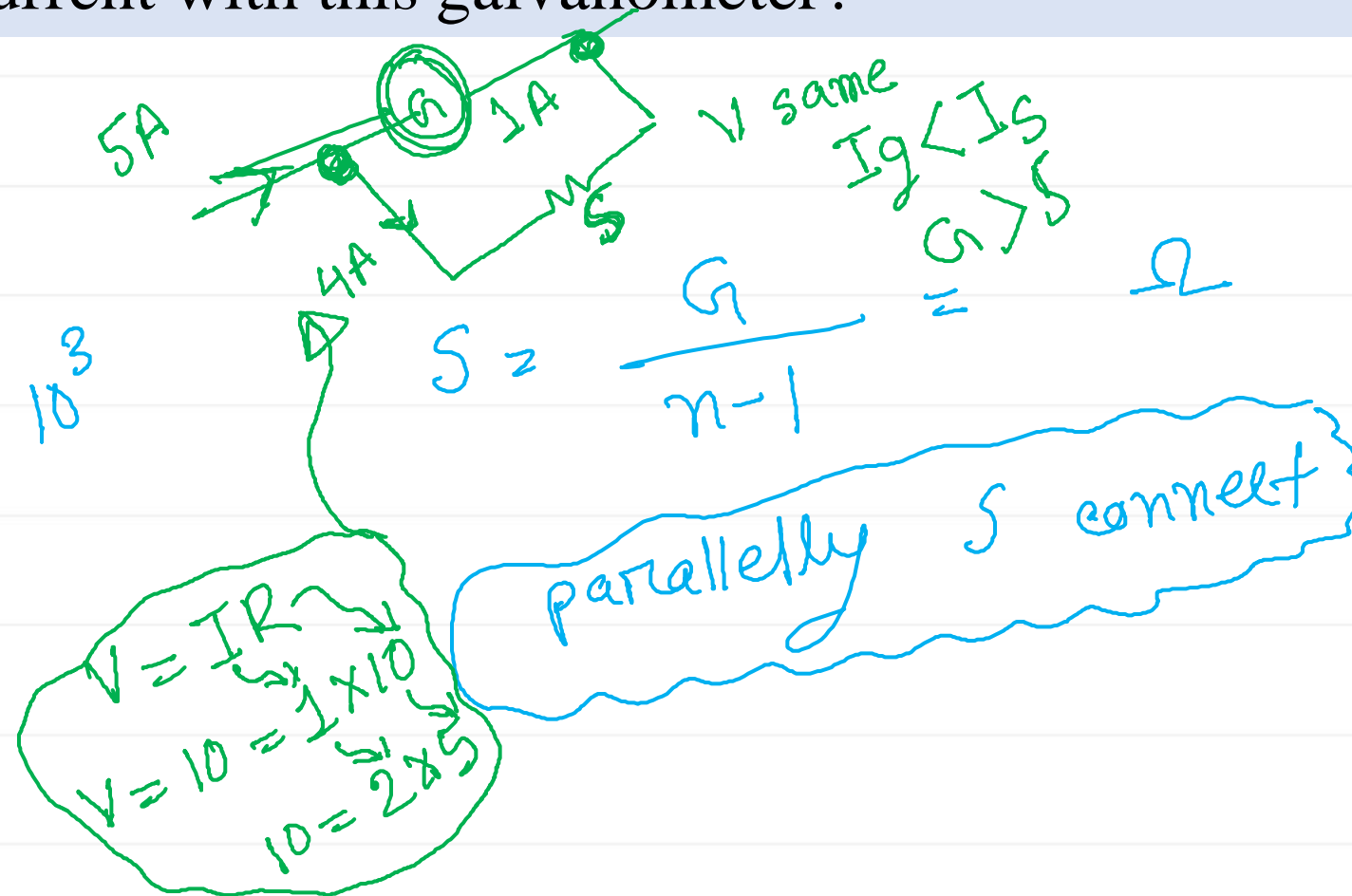
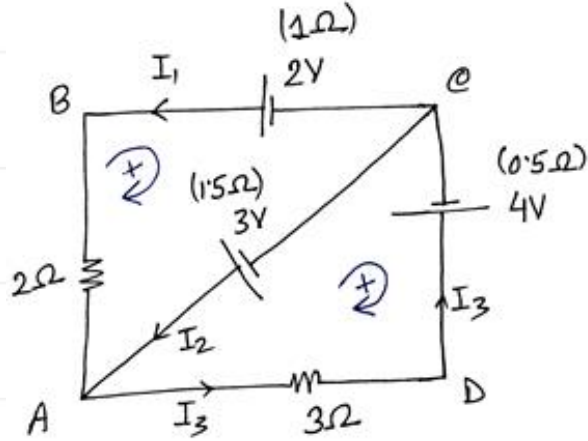
# MATH 04

Calculate current flow through each cell.

In figure,  $E_1 = 2V, E_2 = 3V, E_3 = 4V, r_1 = 1\Omega, r_2 = 1.5\Omega, r_3 = 0.5\Omega, R_4 = 2\Omega$  ও  $R_5 = 3\Omega$ .



ACBA লুপে কির্শফের দ্বিতীয় সূত্র প্রয়োগ করে পাই,

$$I_1 r_1 + I_1 R_4 - I_2 r_2 = E_1 - E_2$$


$$\therefore I_1 (r_1 + R_4) - I_2 r_2 = E_1 - E_2 \dots \dots \dots (i)$$

ADCA লুপে কির্শফের দ্বিতীয় সূত্র প্রয়োগ করে পাই,

$$I_2 r_2 + I_3 R_5 + I_3 r_3 = E_2 - E_3$$

$$\therefore I_2 r_2 + (I_1 + I_2) R_5 + (I_1 + I_2) r_3 = E_2 - E_3 \quad [\because I_3 = I_1 + I_2]$$
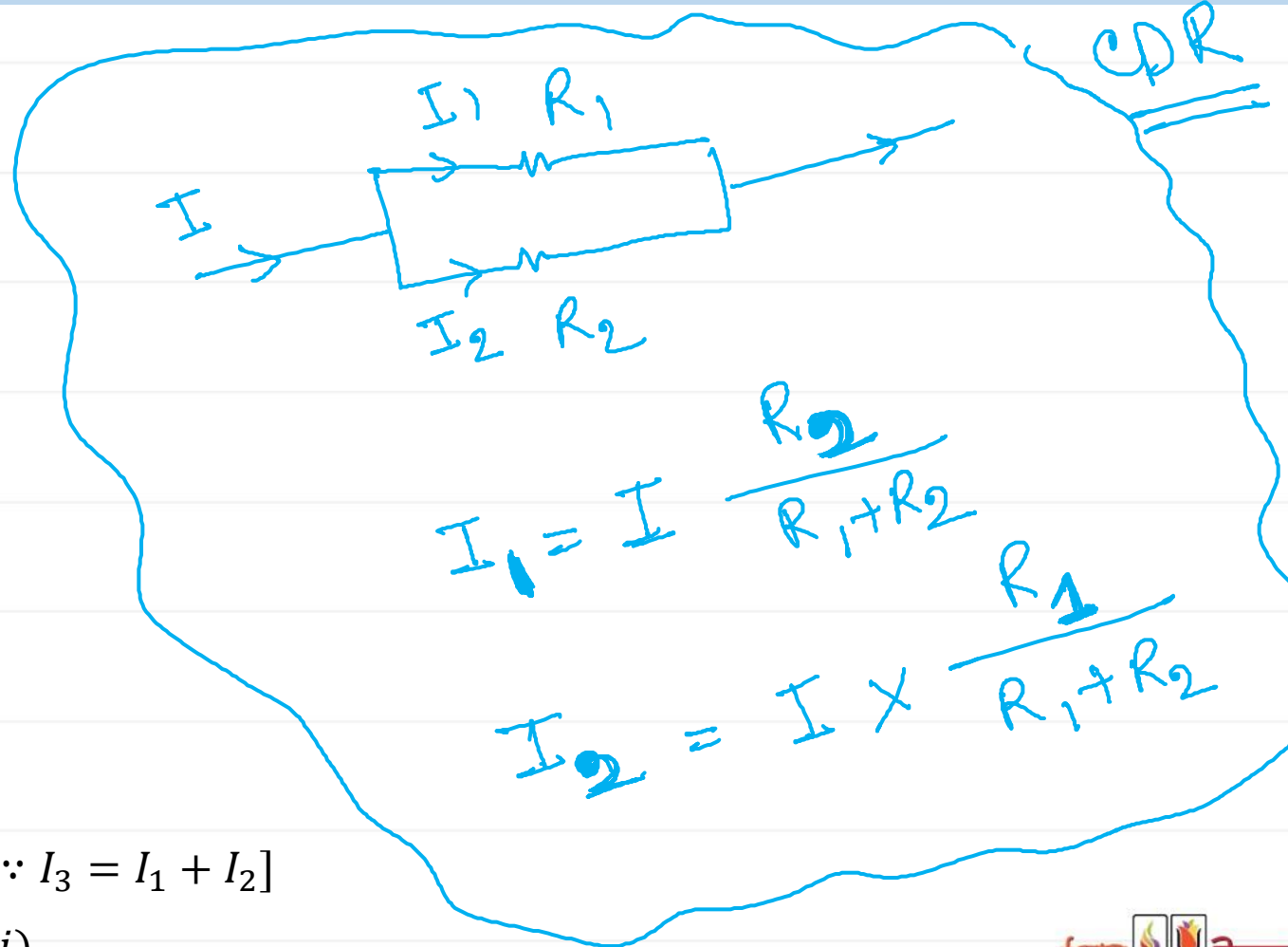
$$\therefore I_1 (R_5 + r_3) + I_2 (r_2 + R_5 + r_3) = E_2 - E_3 \dots \dots \dots (ii)$$



$$I_1 = I \frac{R_2}{R_1 + R_2}$$

$$I_2 = I \times \frac{R_1}{R_1 + R_2}$$



# MATH 04

সমীকরণ (i) ও (ii) এ মানগুলো বসিয়ে পাই,

$$I_1(1 + 2) - I_2 \times 1.5 = 2 - 3$$

$$\text{বা, } 3I_1 - 1.5I_2 = -1$$

$$\text{বা, } 15.I_2 - 3I_1 = 1 \dots \dots \dots (iii)$$

$$\text{এবং } I_1(3 + 0.5) + I_2(1.5 + 3 + 0.5) = 3 - 4$$

$$\text{বা, } 3.5I_1 + 5I_2 = -1 \dots \dots \dots (iv)$$

By solving equation (iii) and (iv)

$$\therefore I_1 = -\frac{26}{81} = -0.321A$$

$$\therefore I_2 = \frac{2}{81} = 0.025A$$

$$\therefore I_3 = I_1 + I_2 = -0.295A$$


value match ✖  
Ishaq 169 page

Here,


$$E_1 = 2V, E_2 = 3V, E_3 = 4V,$$

$$r_1 = 1\Omega, r_2 = 1.5\Omega, r_3 = 0.5\Omega,$$

$$R_4 = 2\Omega, R_5 = 3\Omega.$$

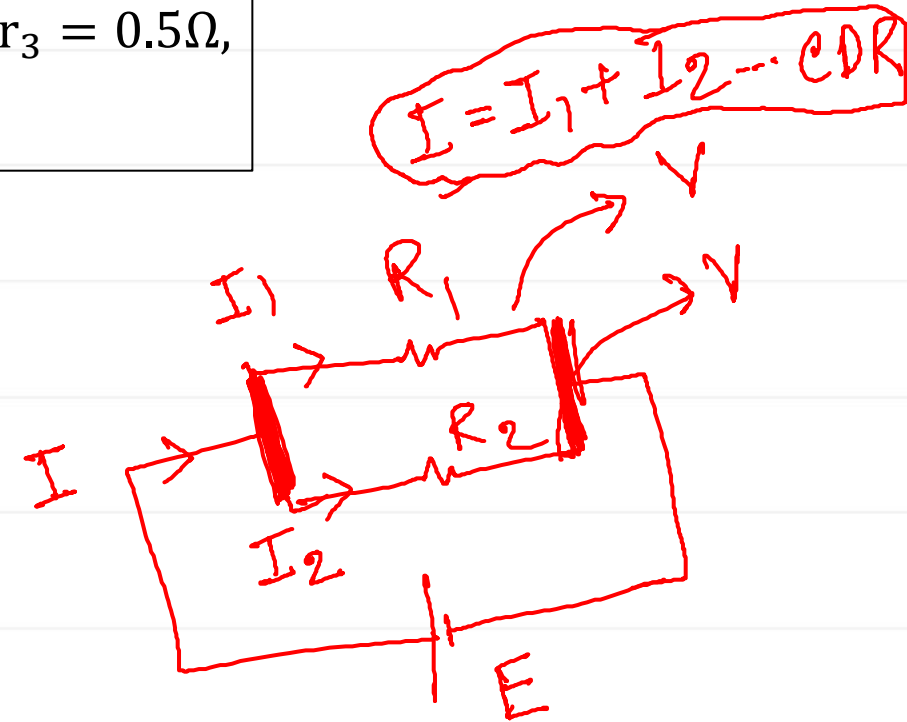

# Math 05

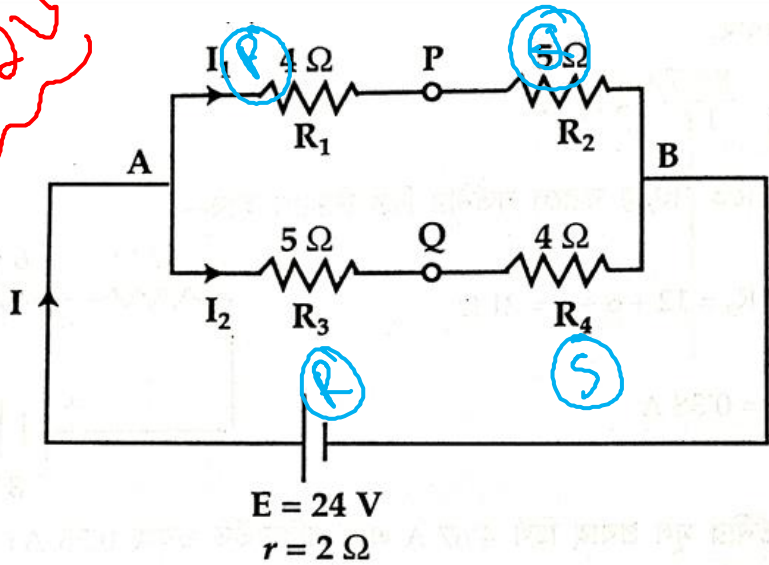

(a) Calculate current flow in the circuit.

(b) If a galvanometer of low resistance is placed between P and Q point, In which direction current will flow?

a) 
$$I = \frac{E}{R_{eq}} = 3.69\text{ amp}$$

$$\left. \begin{array}{l} R_1 + R_2 = 9 \\ R_3 + R_4 = 9 \end{array} \right\} \frac{9}{2} = R_p = 4.5\ \Omega$$

$$r = 2\ \Omega$$

$$R_{eq} = r + R_p$$


b)

$$\frac{P}{Q} \neq \frac{R}{S} \quad \frac{4}{5} \neq \frac{5}{4}$$

$$\frac{P}{R} \neq \frac{Q}{S}$$

not in Equilibrium

# Math 05 continued

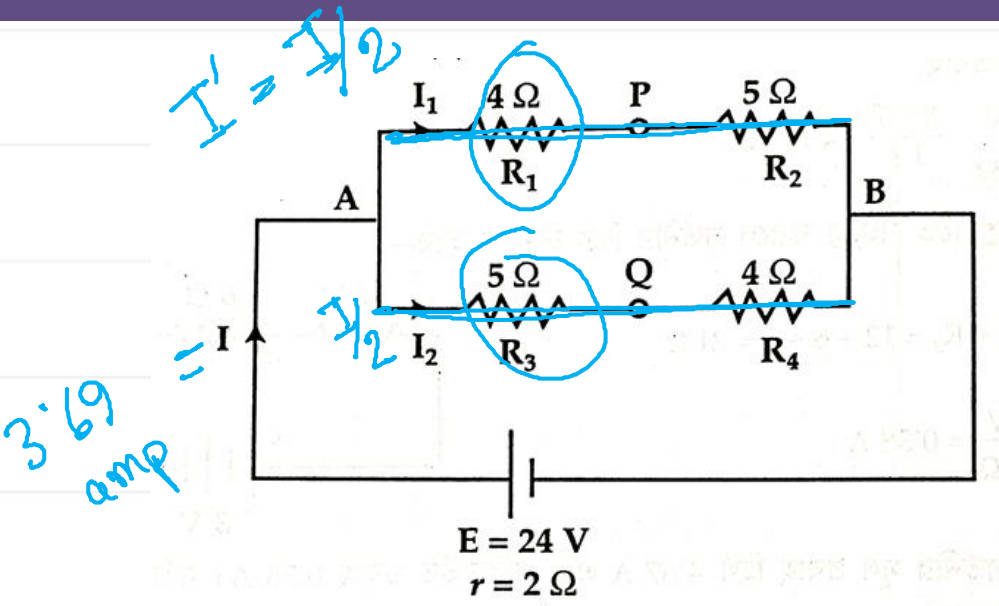

$I = I/2$   
 $3.69\text{ amp}$

$V_{xy} = V_x - V_y$

- (a) Calculate current flow in the circuit.
- (b) If a galvanometer of low resistance is placed between P and Q point, In which direction current will flow?

$\therefore$  not in equilibrium

$\therefore$  flow

$V_A > V_B$   
 $A \rightarrow B$


$I' = \frac{I}{2} = 1.845\text{ amp}$

$V_{AP} = (1.845 \times 4) = 7.38\text{ V} = V_A - V_P$

$V_{AQ} = (1.845 \times 5) = 9.225\text{ V} = V_A - V_Q$

$V_{PQ} = V_{AQ} - V_{AP} = V_P - V_Q$   
 $V_{PQ} = 1.845\text{ V}$   
 $V_P > V_Q$   
 $P \rightarrow Q$
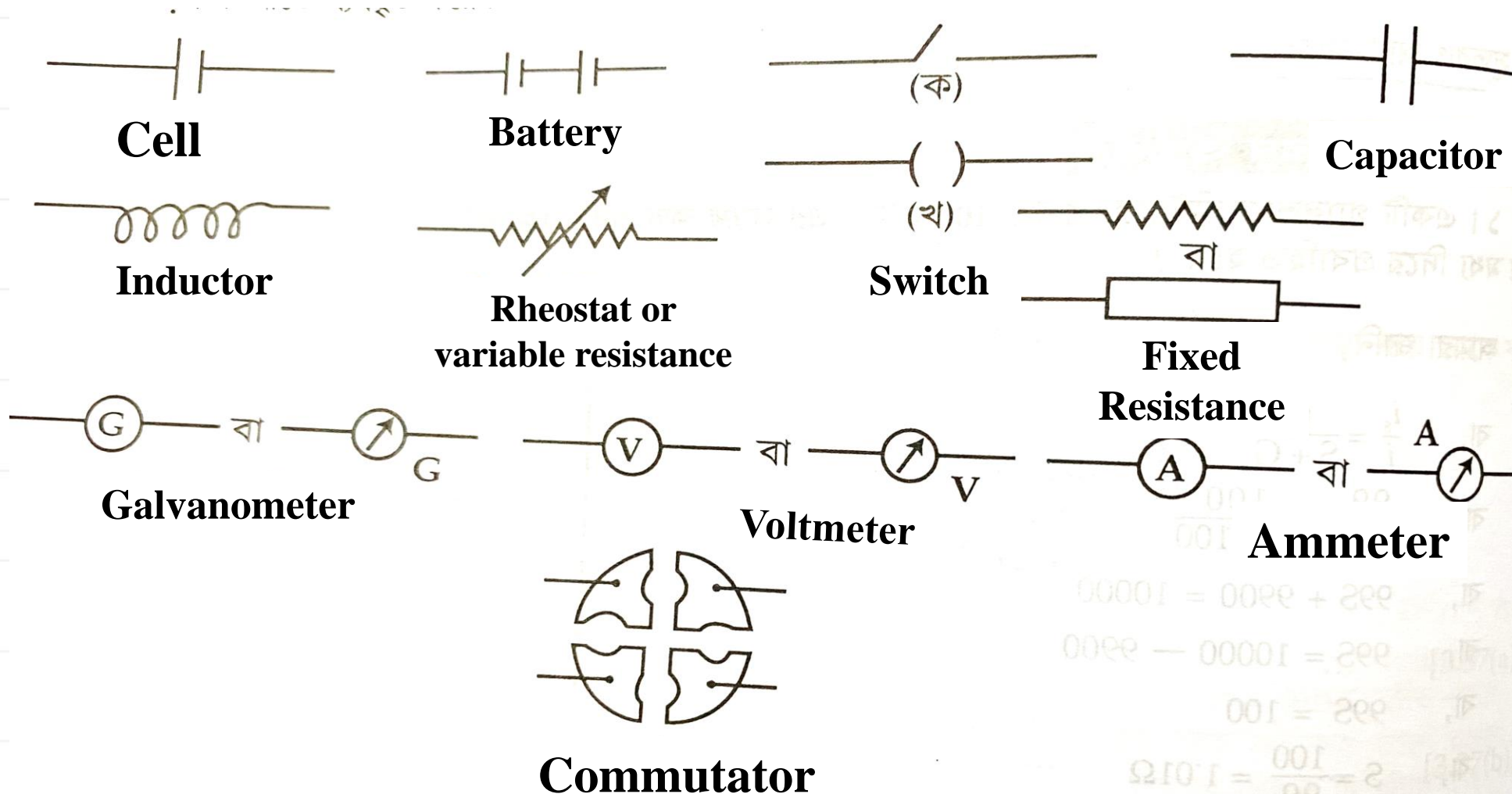
# Few symbols of components used in circuit



লেগে থাকো সৎভাবে,

স্বপ্ন জয় তোমারই হবে

ঊদ্ভাস-উন্মেষ শিক্ষা পরিবার

