

بِسْمِ اللَّهِ الرَّحْمَنِ الرَّحِيمِ

বিস্মিল্লাহির রাহমানির রাহীম



উদ্যান

একাডেমিক এন্ড এডমিশন কেয়ার

# Class 12: Physics 2<sup>nd</sup> Paper (Chapter-3)

## Current electricity


Lecture : P-08

# Today's Topics:

- Electric Cell //
- Internal Resistance and E.M.F  
—  $r$  //  $E$  //
- Relation between internal Resistance and E.M.F
- Mathematical Example  $r$  //  $E$  //
- Combination of cells
- Mathematical Problems //

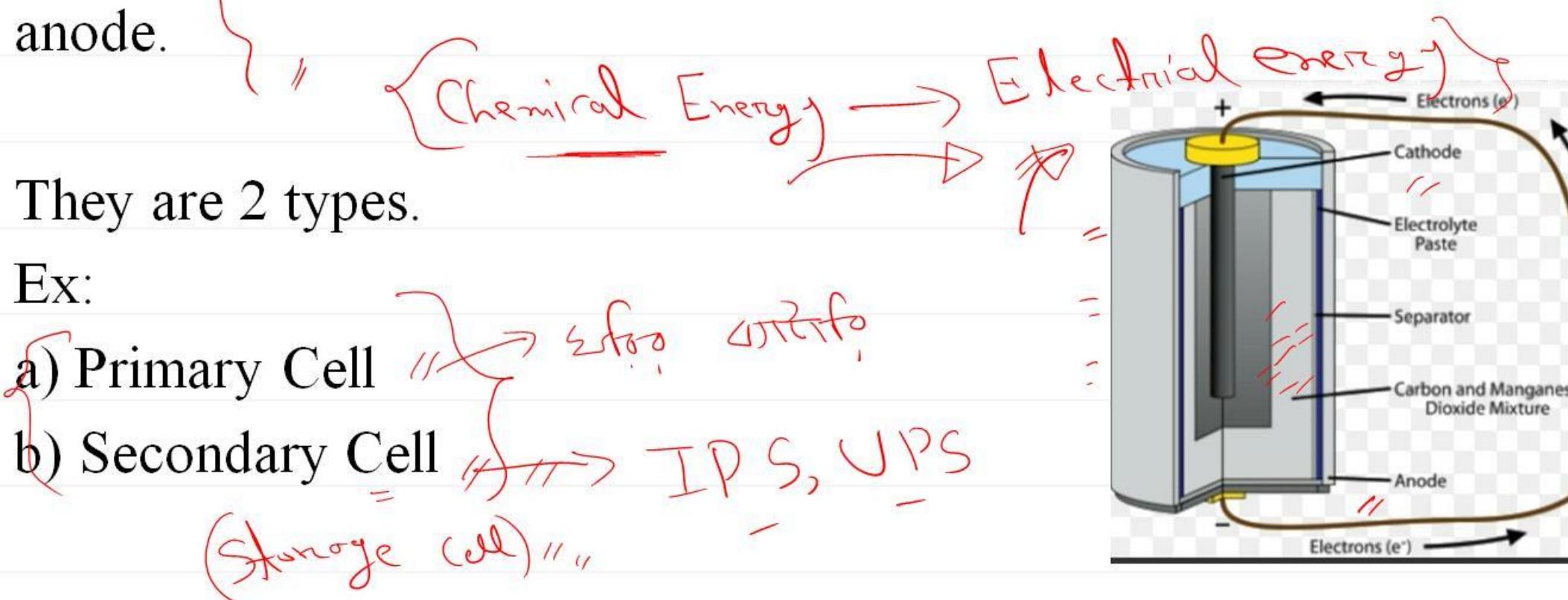
# { Electric Cell }

An electrical cell is an "electrical power supply". It converts stored chemical energy into electrical potential energy, allowing a current to flow from the positive terminal to the negative one via an external circuit. The positive terminal is called a cathode and the negative terminal is called an anode.



# POLL QUESTION 01

Which type of cell is dry cell?

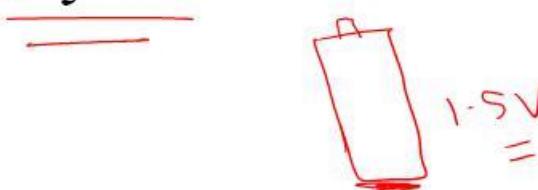

- (a) Secondary Cell
- (b) Primary Cell

# Internal Resistance and E.M.F

## E.M.F

Electromotive force is the characteristic of any energy source capable of driving electric charge around a circuit. It is abbreviated E in the international metric system but also, popularly, as emf.

Voltage difference < E.M.F


## Internal Resistance

Internal Resistance is the resistance which is present within the cell that resists the current flow when connected to a circuit. Thus it causes a voltage drop when current flows through it.

It depends on-

- Chemical properties of materials inside the cell
- Distance between electrodes
- Temperature
- Shape and size of electrodes
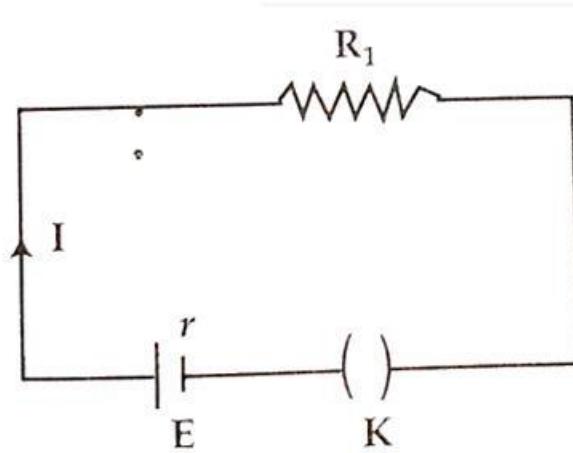
# Relation between internal Resistance and E.M.F



$$R_s = R_1 + r$$

$$E = IR_s$$

$$E = IR_1 + Ir$$

$$E = V + Ir$$


Here,  $V$  = Terminal Voltage

$Ir$  = Lost volt

$$V < E$$

# Internal resistance and electromotive force

Wednesday, July 1, 2020 11:56 PM

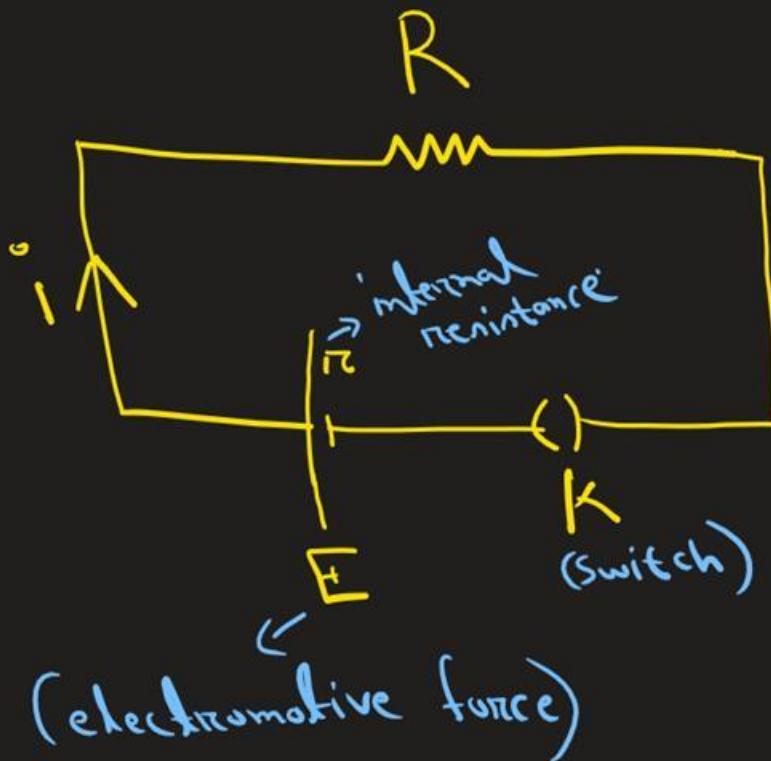

$$E = (IR) + (Ir) \rightarrow \text{Total EMF}$$

Voltage difference ( $V_{out}$ )



$\underbrace{\text{multiple cells}}_{\text{Batteng}}$

$$\begin{aligned} r &= \frac{V}{I} \\ r &= \frac{IR}{I(R+r)} \\ r &= \boxed{r = \frac{R}{R+r}} \end{aligned}$$

## POLL QUESTION 02


In which condition potential difference will be equal to E.M.F?

- (a) Very high current
- (b) ~~Current flow zero~~
- (c) Lesser internal resistance
- (d) Not possible

$$\xrightarrow{\text{Current flow zero}} (I_n = 0)$$


=

$$\checkmark E = V$$

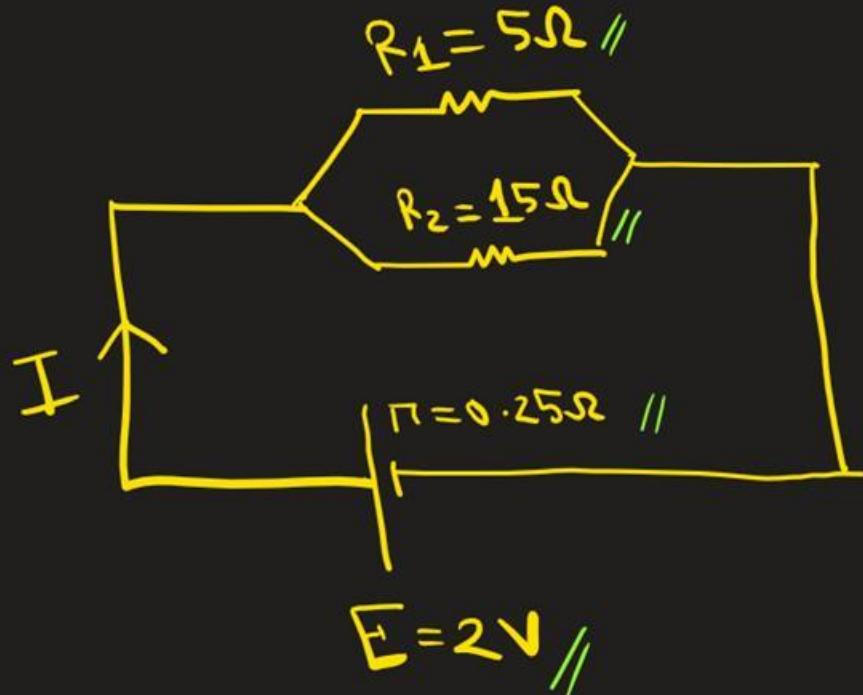

Ques. 9  $I = ?$
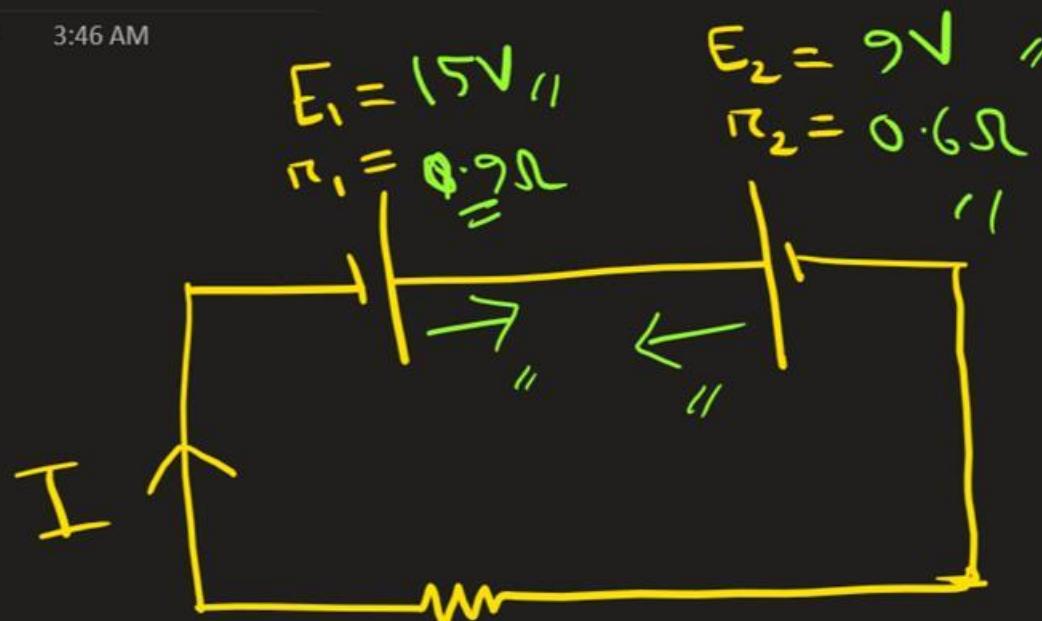
$$\begin{aligned}I &= \frac{V}{R} = \frac{2}{(5 + 15) + 0.25} \\&= \frac{2}{37.5 + 0.25} \\&= \frac{2}{4} = 0.5 \text{ A} \\&\quad (\text{Ans})\end{aligned}$$



$$\parallel R = \frac{1}{\frac{1}{10.5} + \frac{1}{0.9}}$$

Ques.:  $I = ?$

$$\frac{15N}{\rightarrow \square \leftarrow} \rightarrow 6N$$

$$I = \frac{V}{R}$$

$$= \frac{15 - 9}{10.5 + 0.9 + 0.6}$$

$$= \frac{6}{12} = 0.5A$$


(Ans)

# POLL QUESTION 03

How much current is flowing through  $10\text{ ohm}$  ?

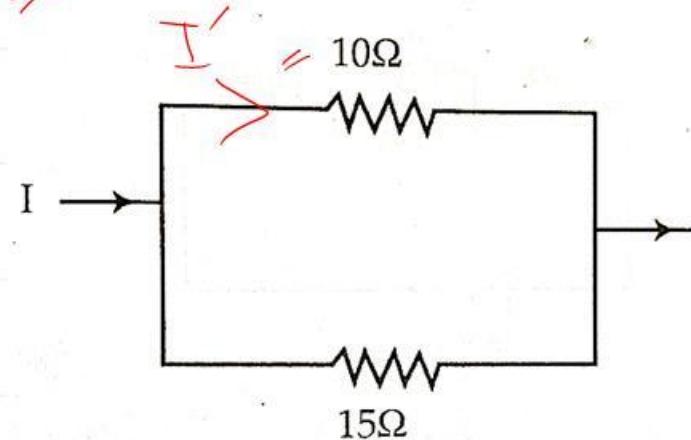- (a) 0.6
- (b) 0.5
- ~~(c) 0.6 I~~
- (d) 0.5 I


$$I' = I \left( \frac{10^{-1}}{10^{-1} + 15^{-1}} \right)$$




$$\begin{aligned} &= I \times 0.6 \\ &= 0.6I \end{aligned}$$
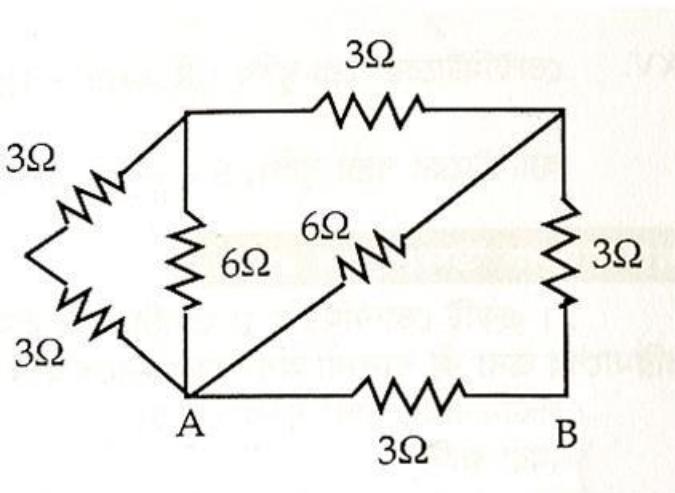
# MATH 03

Calculate equivalent resistance  $R_{AB}$



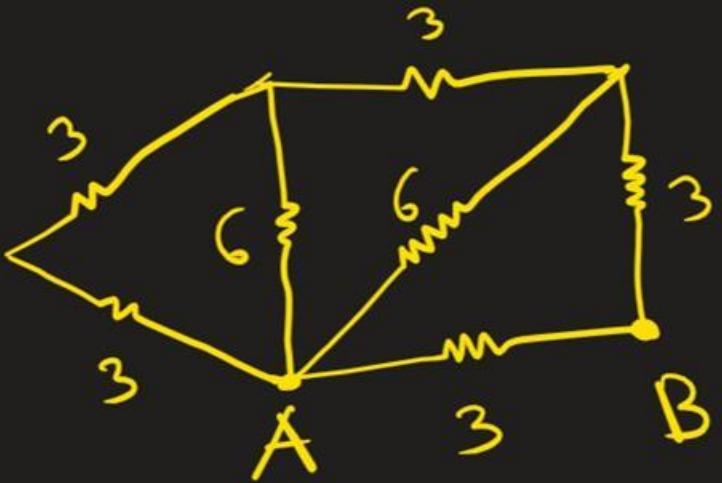

Quer.:  $\underline{\underline{R_{AB}}}$  = ?


Soluti:

$$\begin{aligned}
 & \left\{ \left[ \left\{ \left( (3+3) // 6 \right) + 3 \right\} // 6 \right] + 3 \right\} // 3 \\
 &= \left[ \left\{ \left( (6//6) + 3 \right) // 6 \right\} + 3 \right] // 3
 \end{aligned}$$

$$\begin{aligned}
 &= \left\{ (0 + 3) // 3 \right\} \\
 &= 6 // 3 = \textcircled{2\Omega} \\
 &\quad \text{(Ans.)}
 \end{aligned}$$

# MATH 04


Calculate equivalent resistance

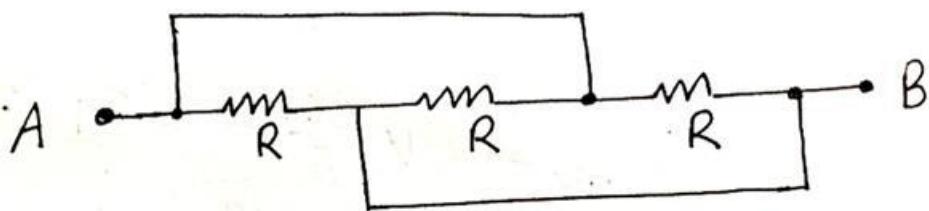

# Math 4.1 + point concept + (R/n formula)


Thursday, July 2, 2020

3:49 AM

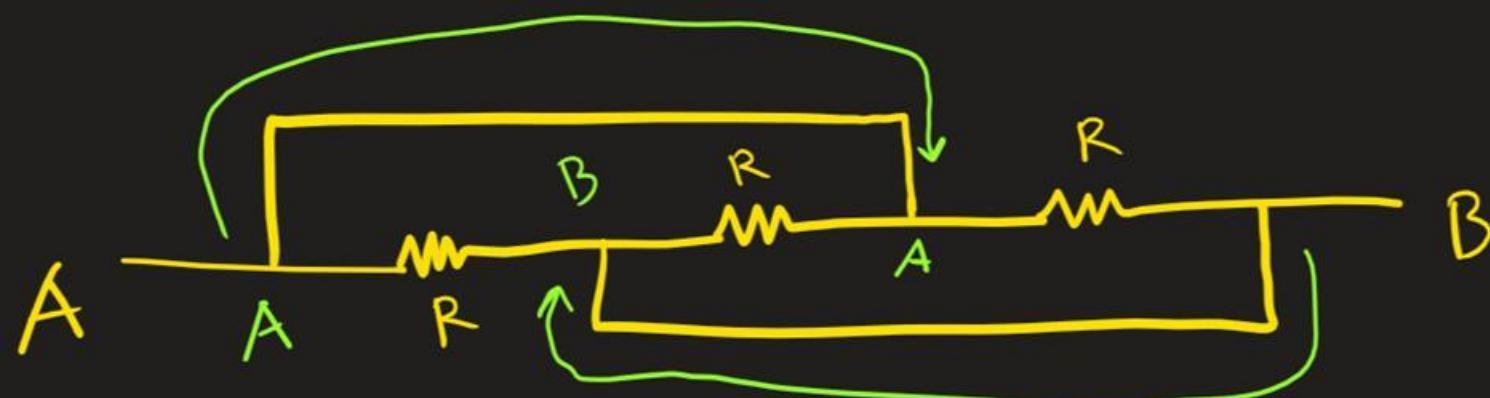


Ques.:  $R_{AB} = ?$

(point concept of Resistance)

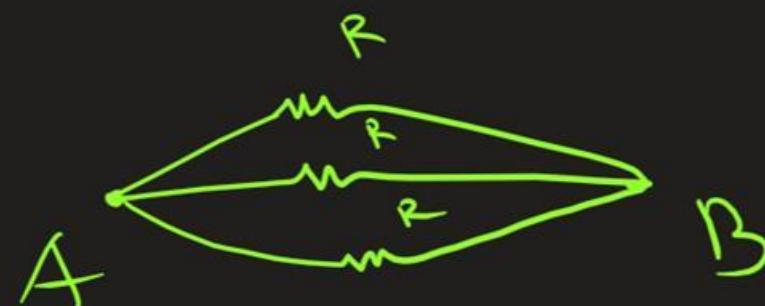

$$\text{So, } R_{AB} = \frac{R}{3}$$

(Ans)

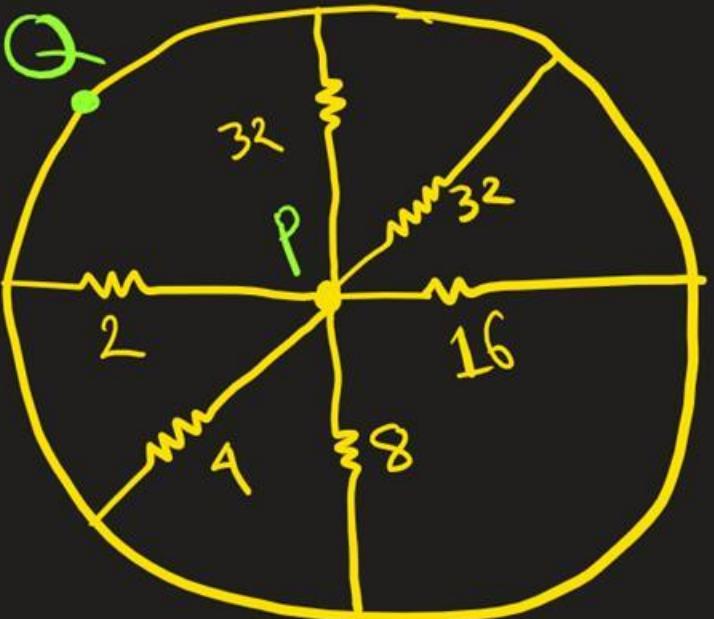

Ques. :  $R_{PQ} = ?$

Soln. All the resistors are in parallel connection.

So,

$$\frac{1}{R_{PQ}} = \frac{1}{32} + \frac{1}{32} + \frac{1}{16} + \frac{1}{8} + \frac{1}{4} + \frac{1}{2}$$

$$\Rightarrow R_{PQ} = 1\Omega$$

(Ans)

# POLL QUESTION 04

Calculate current flow.


(a) 0.57 amp

~~(b) 1.75 amp~~

(c) 0.25 amp

(d) 4 amp


$$I = \frac{V}{R}$$

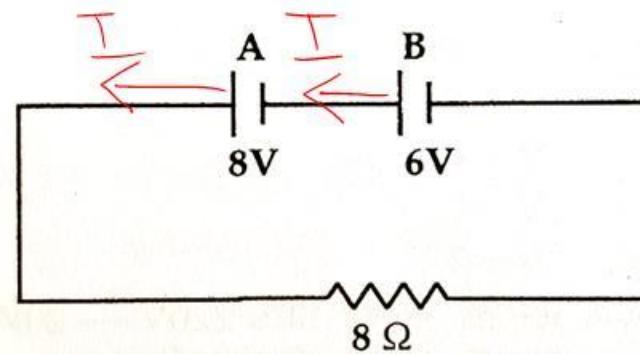

$$= \frac{8+6}{8} = \frac{14}{8} = \frac{7}{4} = 1.75A$$

# Increasing the range of voltmeter

Thursday, July 2, 2020 4:01 AM

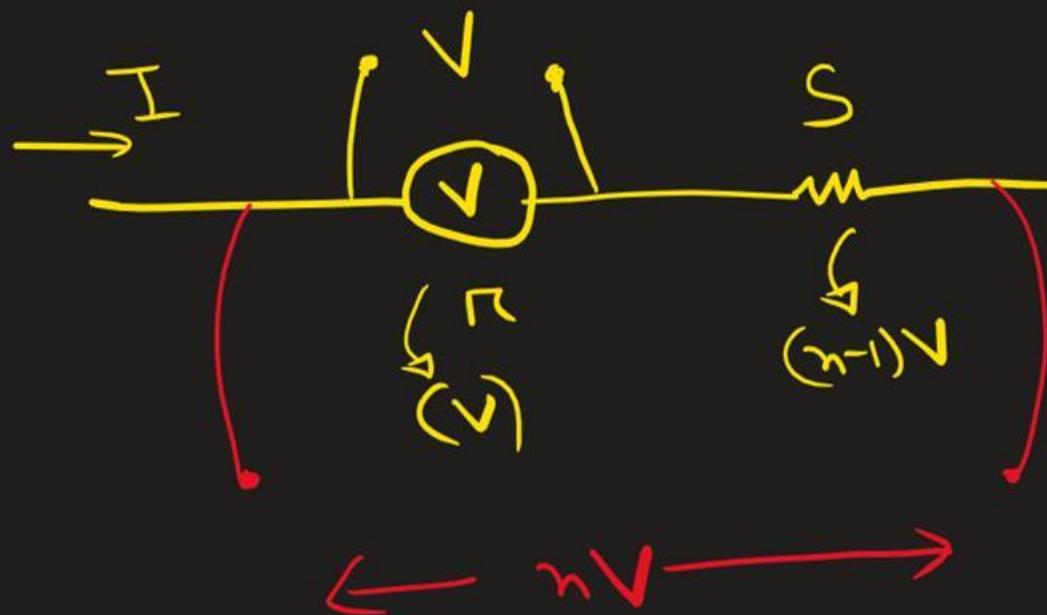

a shunt of  $S$  ohm is required

to connect in Series with Voltmeter to  
measure Voltage  $n$  times.

$$\left. \begin{array}{l} V = IR \\ (n-1)V = IS \end{array} \right\} \Rightarrow \frac{(n-1)V}{V} = \frac{IS}{IR} \Rightarrow S = (n-1)R$$

# MATH 05

A voltmeter of 1000 ohm internal resistance can measure 15 volt. How can it measure 150v ?

A voltmeter of 1000 ohm internal resistance can measure upto 15 volt. What measure should be taken to measure 150 volt by the same voltmeter?

Soln:


$$R = 1000\Omega ; V = 15V ; nV = 150V$$
$$\therefore n = 10$$

$$S = (n-1)R = (10-1) \times 1000 = \boxed{9000\Omega} \text{ in Series} \quad (\underline{\text{Am}})$$

# Increasing the range of ammeter

Thursday, July 2, 2020

4:01 AM

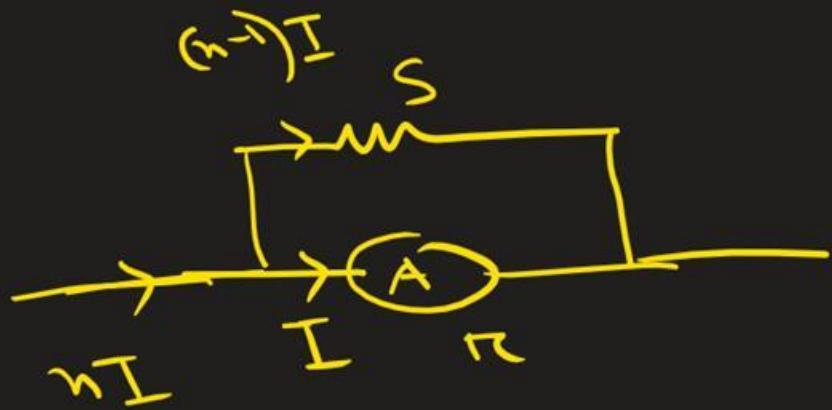

$$V = I_n = (n-1)I \cdot S$$

$$\Rightarrow I_n = (n-1)I \cdot S$$

$$\Rightarrow S = \frac{n}{n-1}$$

in parallel to increase the  
range of Ammeter by  $n$  times

# MATH 06

An ammeter of 2 ohm internal resistance can measure upto 0.2 amp current. How can it measure 2 amp current?

An ammeter of  $2\Omega$  internal resistance can measure upto  $0.2\text{Amp}$ , what measure should be taken to measure  $2\text{Amp}$  by the same Ammeter?

Soln:  $R = 2\Omega$ ;  $I = 0.2\text{A}$ ;  $nI = 2\text{A}$

$$\text{So, } n = 10$$

$$S = \frac{R}{n-1} = \frac{2}{10-1}$$

(in parallel)

$$= \boxed{\frac{2}{9}\Omega}$$


(Am)

# Combination of cells

There are 3 types of combination. These are-

- (a) Series combination
- (b) Parallel combination
- (c) Mix combination


# Series combination

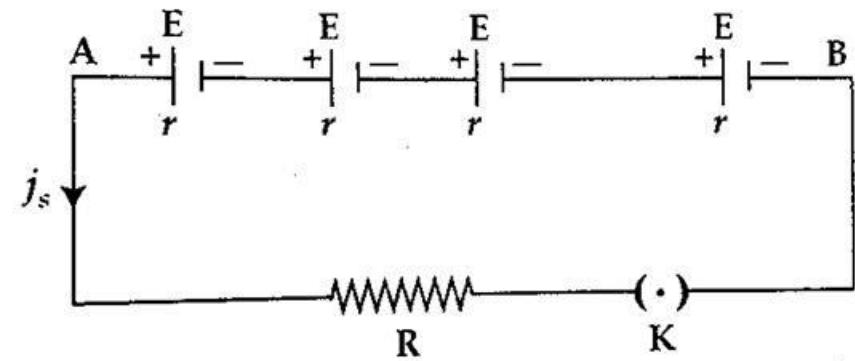
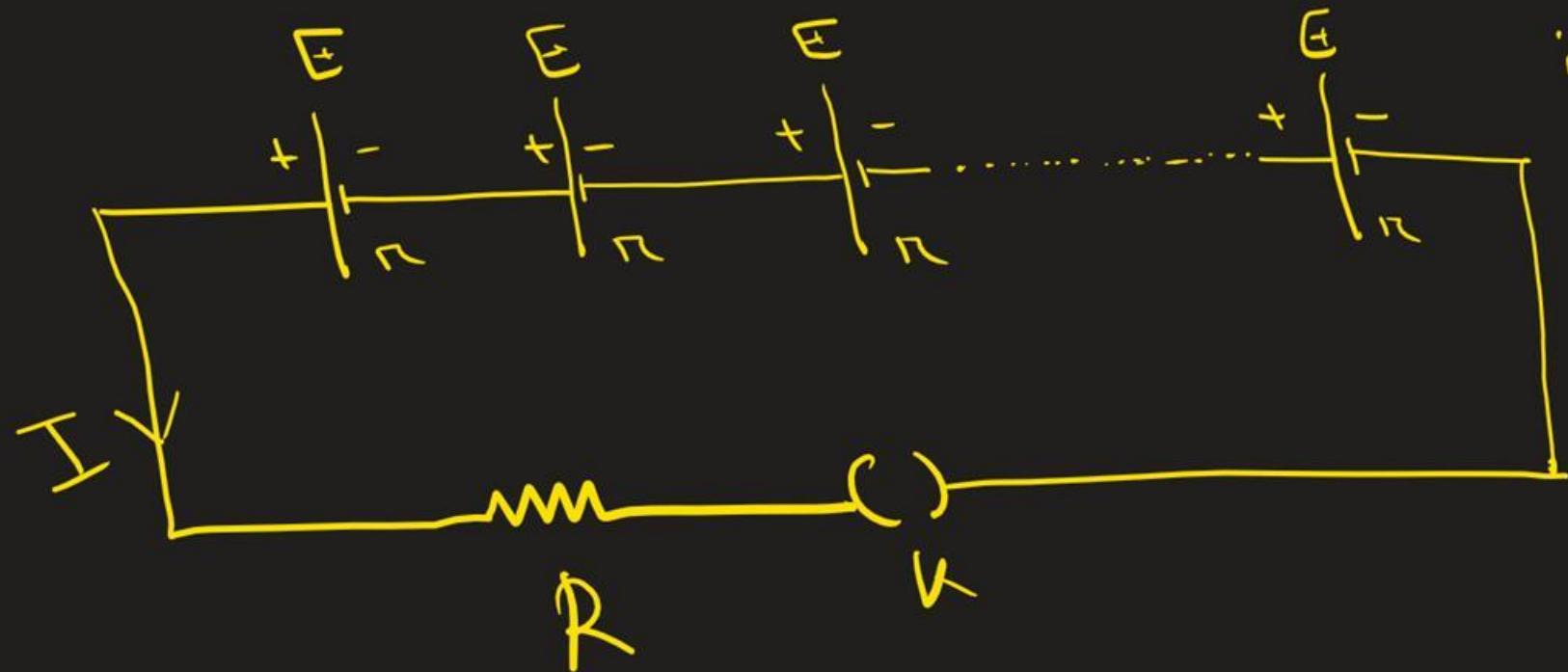
## Series combination

Thursday, July 2, 2020 4:04 AM

(n no. of cells are  
in Series connection)



$$I = \frac{nE}{R + n\tau} ; \text{ when, } R \gg \tau, \quad R + n\tau \approx R$$

$$\text{So, } I \approx \frac{nE}{R}$$

if 1 cell,  $I = E/R$   $\rightarrow$  n times current

[ so, we should use  
series combination  
when  $R \gg \tau$  ]

# POLL QUESTION 06


if  $E=E_1=E_2=E_3$  and resistance is  $R$ , calculate  $I$ .

(a)  $\frac{3E}{3R+r}$


(b)  $\frac{E}{3R+r}$

(c)  $\frac{3E}{R+3r}$

(d)  $\frac{3E}{3R+3r}$

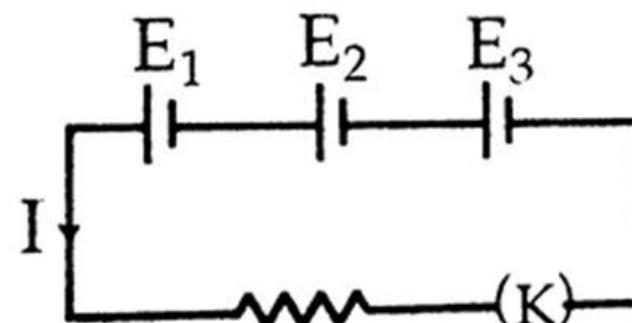


# Parallel Combination

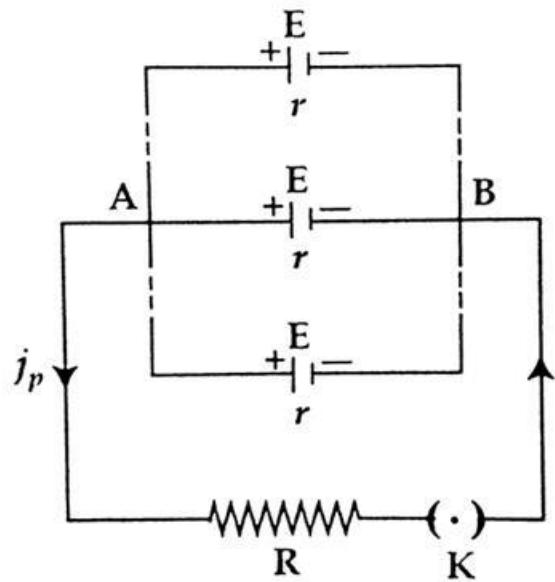

## Parallel combination

Thursday, July 2, 2020 4:06 AM

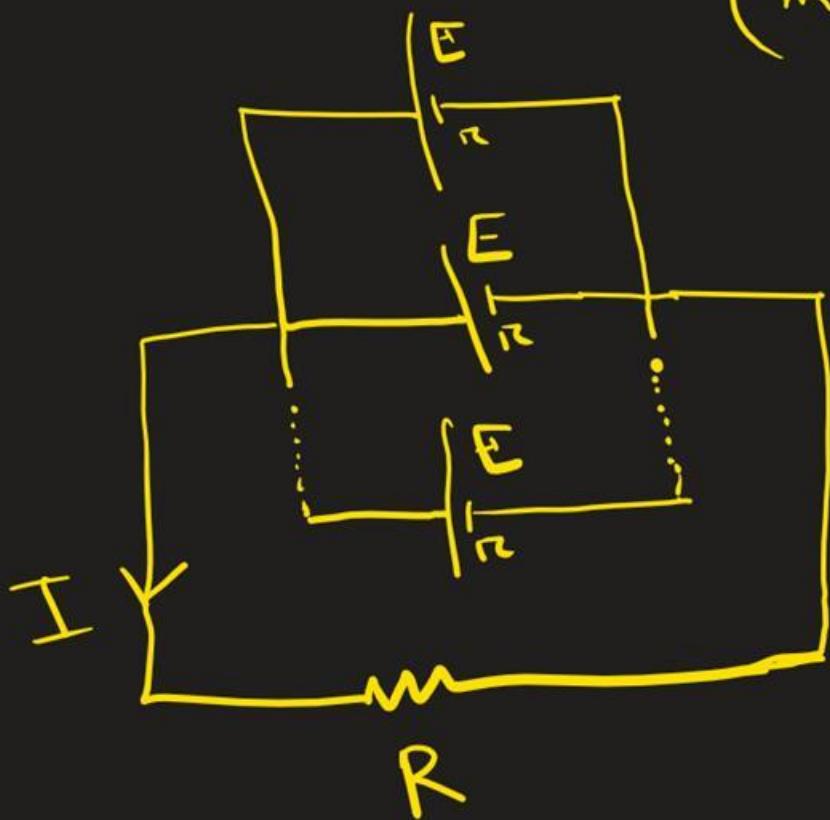

(m no. of cells are in parallel connection)

$$I = \frac{E}{R + r/m} = \frac{mE}{mr + R}$$


when,  $R \ll r$ ,  $mr + R \approx mr$

$$\text{So, } I \approx \frac{mE}{r}$$

if one cell,  $I = E/r$ . So, m times current  
So, we parallel combin', only when,  $R \ll r$

## Mixed combination

Thursday, July 2, 2020 4:09 AM

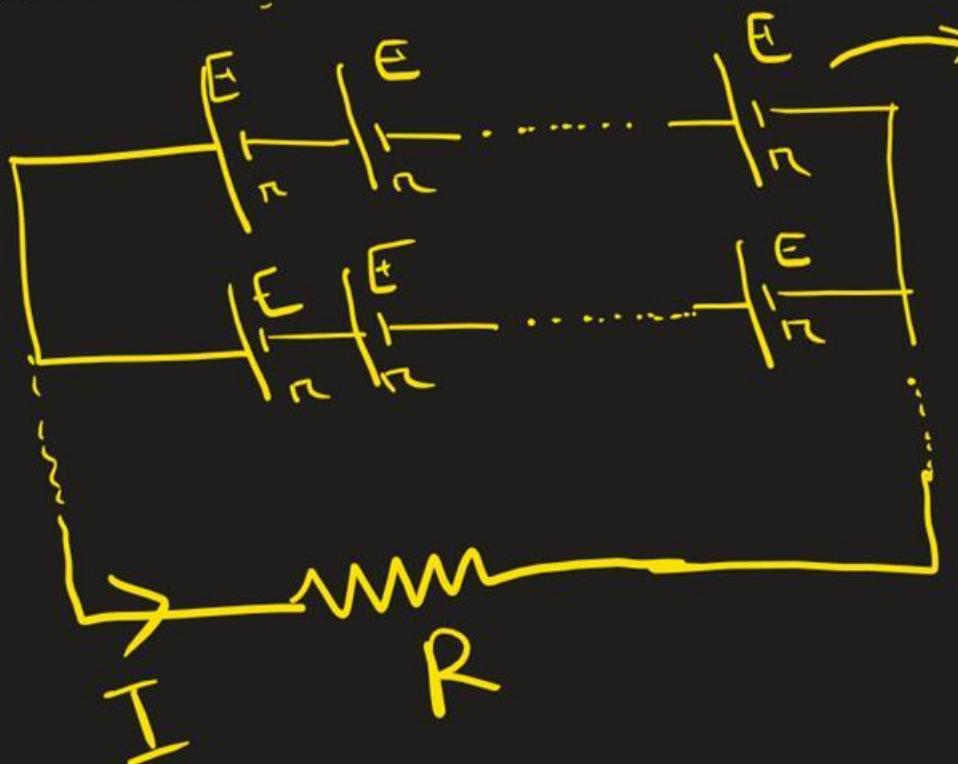


[in each line,  $n$  no. of cells are in Series connection]

[ $m$  no. of lines, each of which contains  $n$  no. of cells in Series ]

$$I = \frac{nE}{R + \frac{nr}{m}} = \frac{mnE}{mR + nr}$$

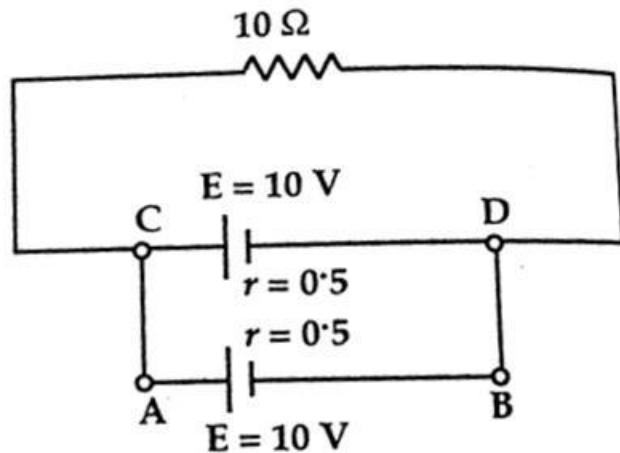
# Mix Combination

Calculate power dissipated in 10 ohm resistor.



# Mix comb math

Thursday, July 2, 2020 4:12 AM

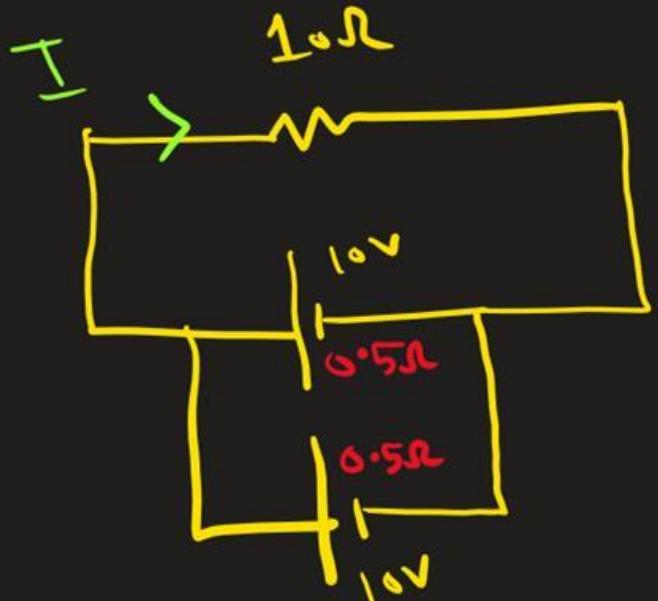

$$\text{Soh}^n: \quad I = \frac{10}{10 + \frac{0.5}{2}} = 0.9756A$$

$$H = I^2 R t \quad \begin{matrix} \text{if nothing specified} \\ \rightarrow \end{matrix}$$

$$= (0.9756)^2 \times 10 \times (1)$$

$$= 9.506 \text{ J/second} \\ (\text{Amm})$$

Ques.: How much heat will  
be produced in 1Ω resistor?

# MATH 07

30 electric cells of 5 ohm internal resistance and 10 v emf are equally distributed in 5 branches. 30 ohm resistor is added with them in parallel. Calculate current flow through 30 ohm resistor.

30 electric cells each having 10V EMF and  $5\Omega$  internal resistance are equally distributed to 5 branches.  $30\Omega$  of resistance is connected in parallel to them. What will be the current flowing through  $30\Omega$  resistor?

Sln:  $R = 5\Omega$ ;  $E = 10V$ ;  $m = 5$ ;  $mn = 30$ ;  $R = 30\Omega$

$$\boxed{n=6}$$

Now,  $I = \frac{nE}{R + nR/m} = \frac{mnE}{mR + mn} = \frac{5 \times 6 \times 10}{(5 \times 30) + (6 \times 5)} = 1.67 A$   
 $(Am)$

ଲେଗେ ଥାକୋ ସଂଭାବେ,  
ସ୍ଵପ୍ନ ଜୟ ତୋମାରଙ୍କ ହବେ

ଉତ୍ତରାସ-ଉତ୍ତରେଷ ଶିକ୍ଷା ପରିବାର

